

Lecture 3: General Purpose Processor Design

CSCSE 6651

Advanced VLSI Systems

Instructor: Saraju P. Mohanty, Ph. D.

NOTE: The figures, text etc included in slides are borrowed from various books, websites, authors pages, and other sources for academic purpose only. The instructor does not claim any originality.



Lecture Outline

- General Purpose Processor
- Program Execution
- Construction of a Simple MIPS Processor
- Single Cycle Processor
- Multicycle Processor
- Pipelined Processor



Levels of Representation

High Level Language Program

Compiler

Assembly Language Program

Assembler

Machine Language Program

Machine Interpretation



```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;
```

```
lw $15, 0($2)
```

```
lw $16, 4($2)
```

```
sw      $16, 0($2)
```


```
sw      $15, 4($2)
```

```
0000 1001 1100 0110 1010 1111 0101 1000
1010 1111 0101 1000 0000 1001 1100 0110
1100 0110 1010 1111 0101 1000 0000 1001
0101 1000 0000 1001 1100 0110 1010 1111
```

```
ALUOP[0:3] <= InstReg[9:11] & MASK
```



Execution Cycle

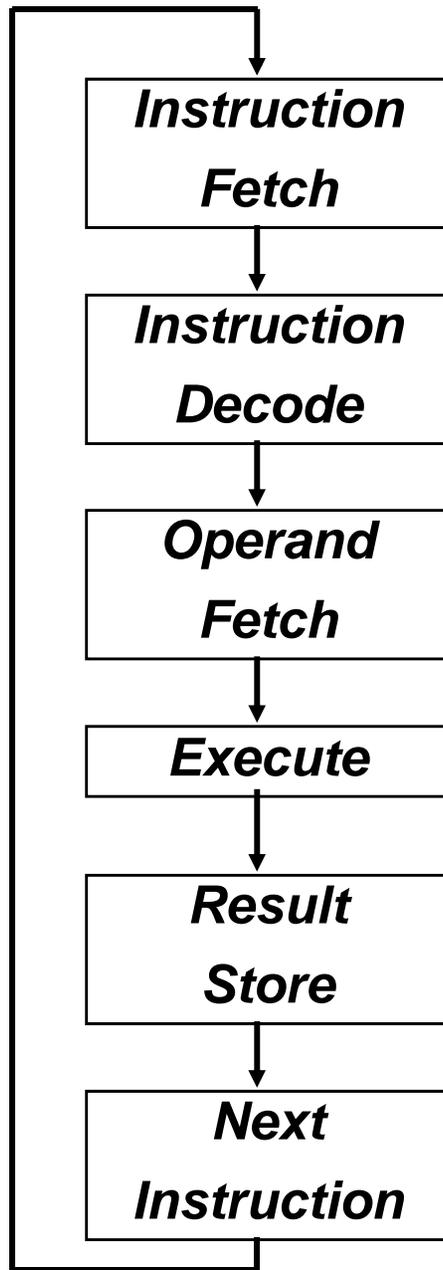

Obtain instruction from program storage


Determine required actions and instruction size

Locate and obtain operand data

Compute result value or status

Deposit results in storage for later use

Determine successor instruction

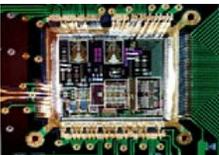

The Processor: Datapath & Control

- Let us look at an implementation of the MIPS
- Simplified to contain only:
 - memory-reference instructions: `lw`, `sw`
 - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `sllt`
 - control flow instructions: `beq`, `j`


Generic Implementation:

- use the program counter (PC) to supply instruction address
- get the instruction from memory
- read registers
- use the instruction to decide exactly what to do




More Implementation Details

- Abstract / Simplified View:

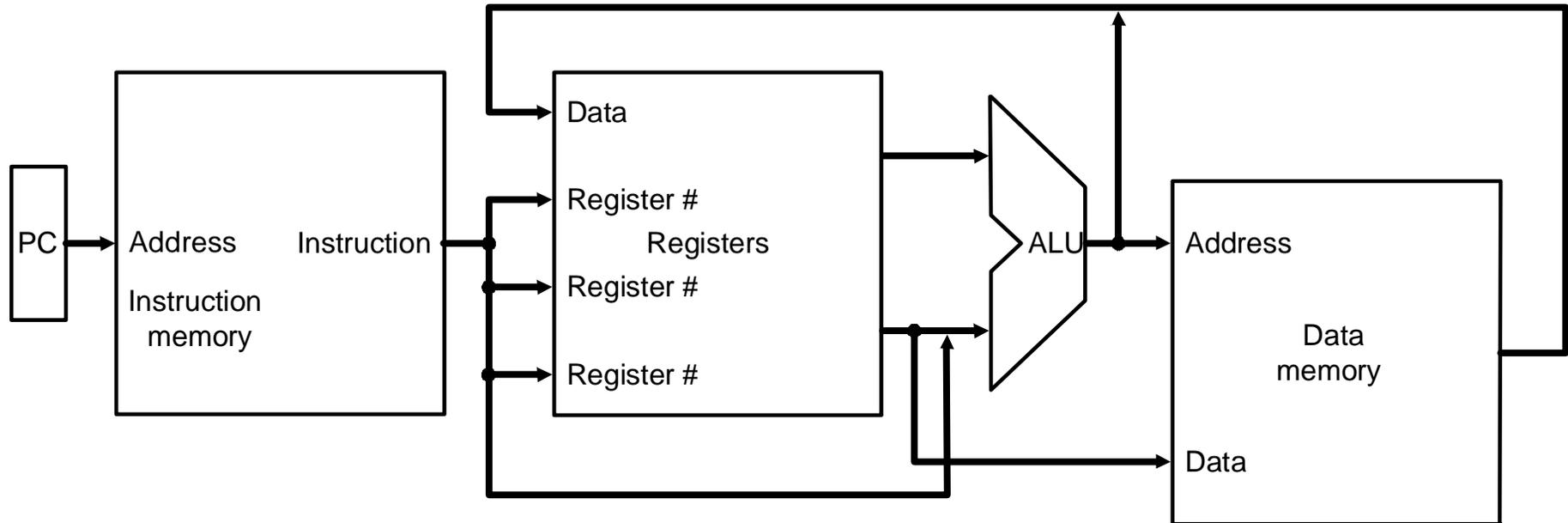


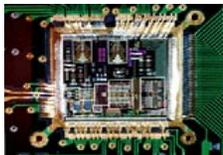- Two types of functional units:
 - elements that operate on data values (combinational)
 - elements that contain state (sequential)





Register File: Read Operation

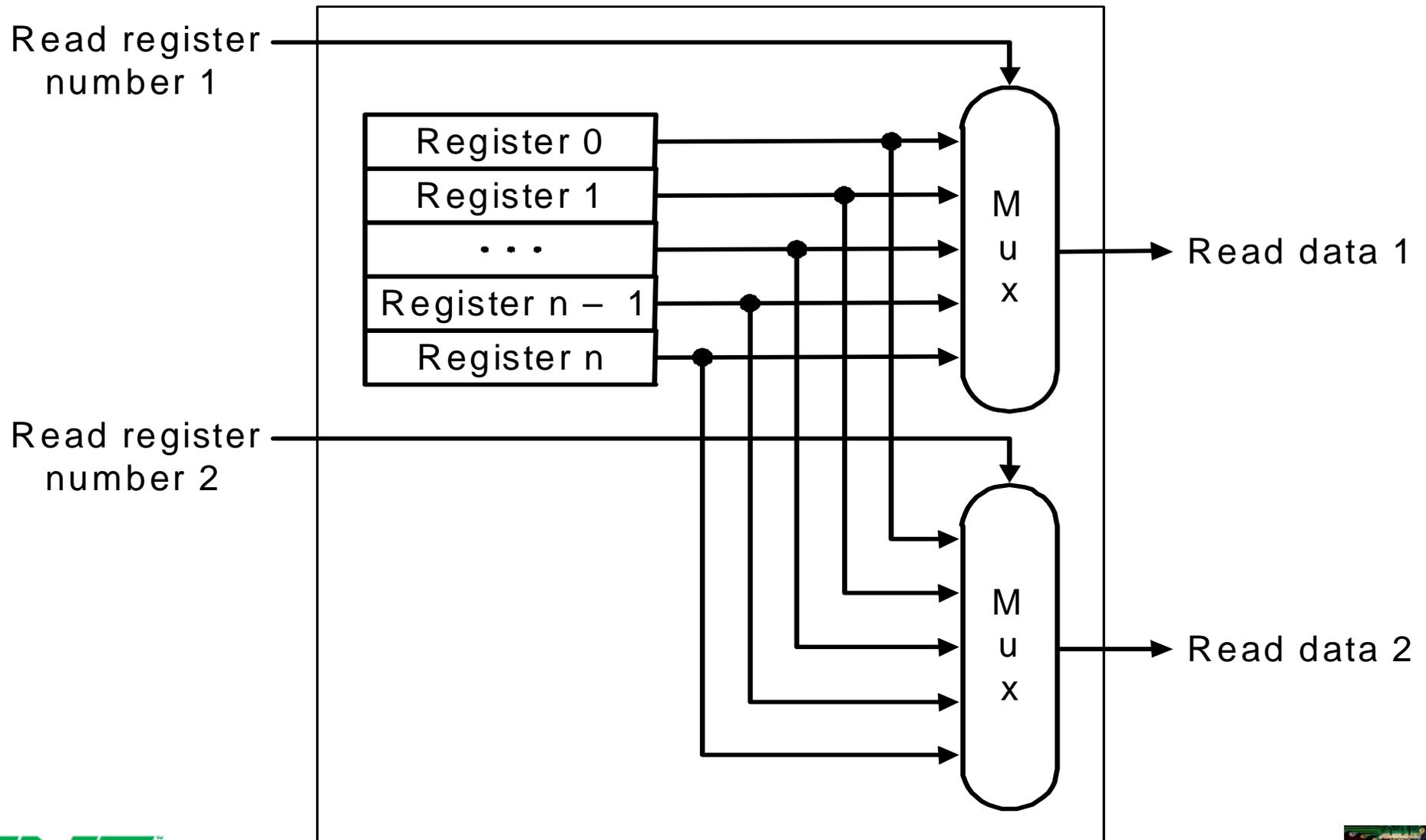- Built using D flip-flops (Combinational in nature)




Register File: Write Operation

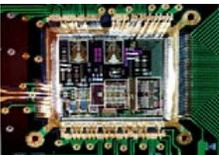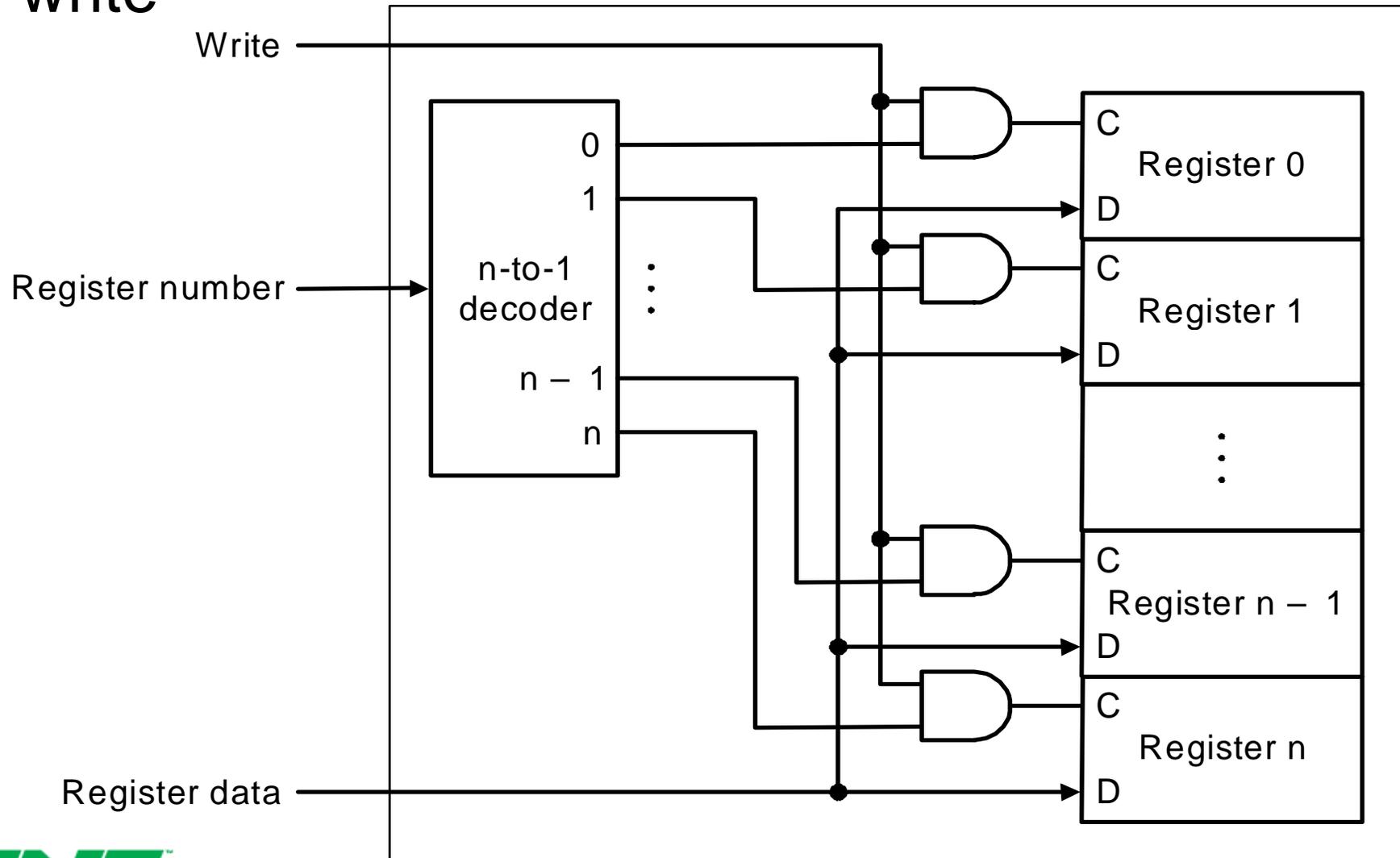
- We still use the real clock to determine when to write



Register File: Block Diagram

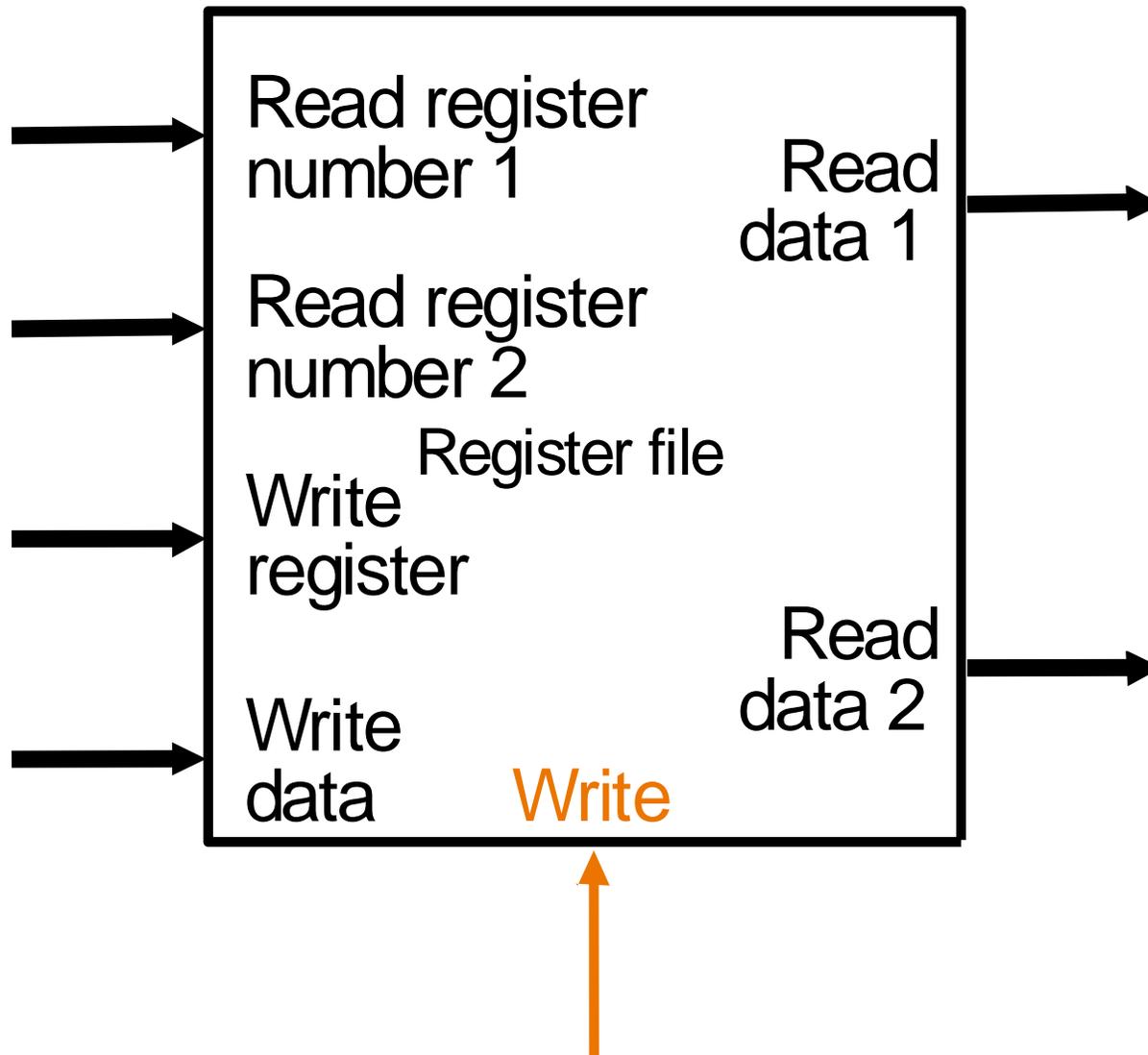

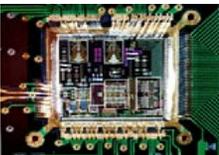- Three Address ports
- One Data Input Port
- Two Data Output Ports
- One Write Control Signal




Functional Units - I

a: *Instruction Memory*


After an instruction address is put, the instruction residing at the address appears at the output port

b: *Program Counter* -- A simple up counter


c: *Adder* -- A 2's complement adder

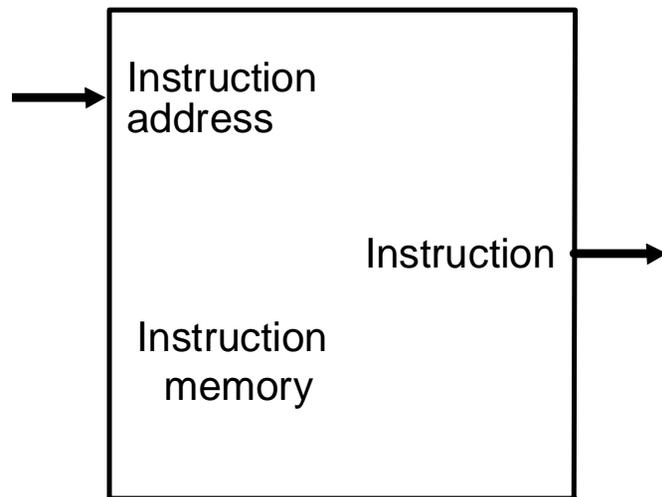


a. Instruction memory

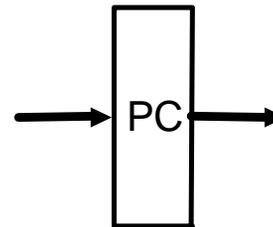

b. Program counter

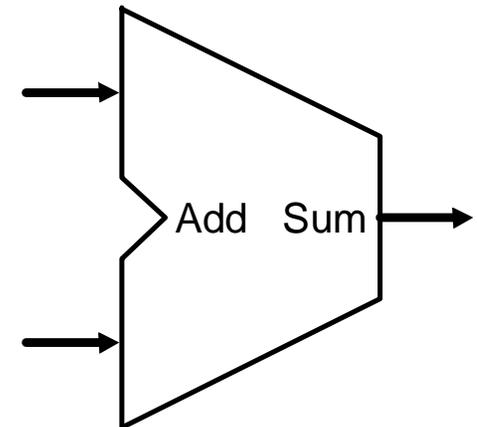

c. Adder

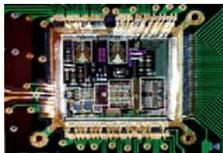

Functional Units - II


a: Register File

It's construction, read, and write operations as discussed previously

b: ALU (Arithmetic & Logic Unit)


Recall the ALU design we have discussed in last two classes

Note the "Zero" output

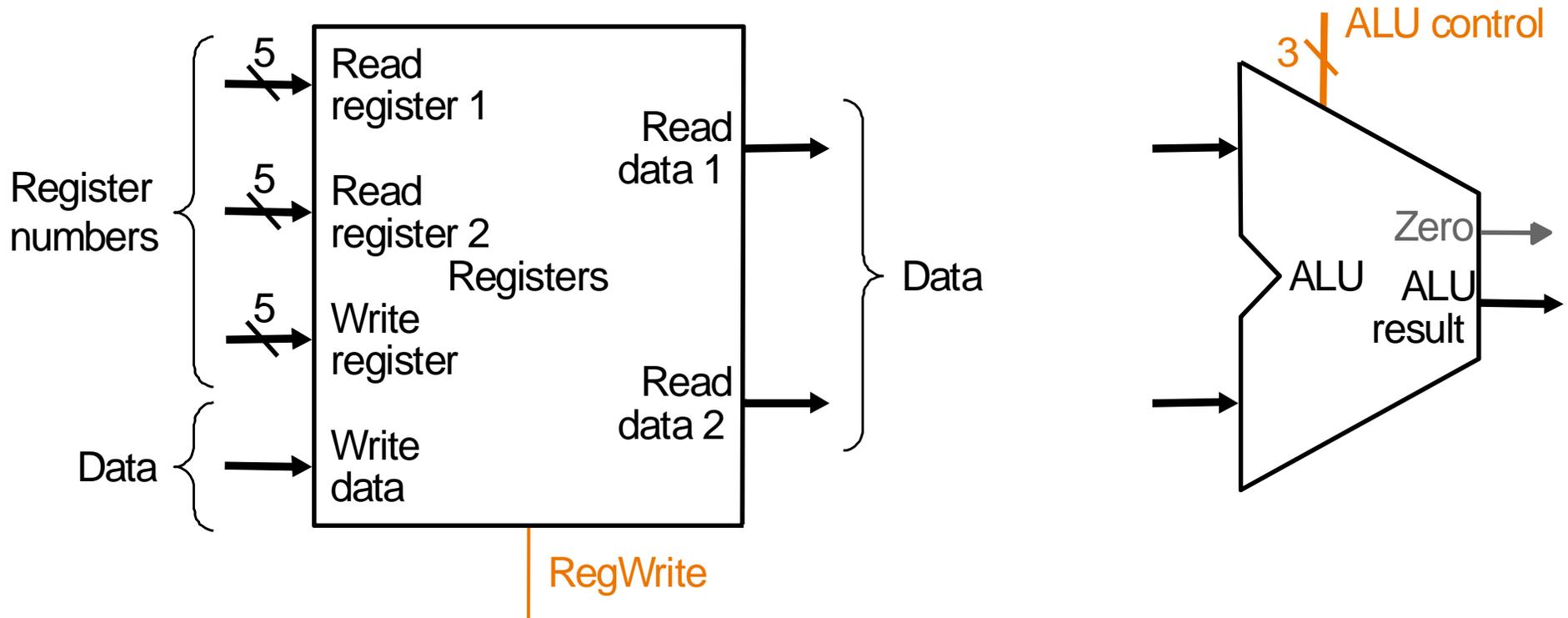

a. Register File

b. ALU

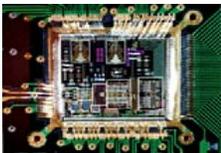

Functional Units -III

a: *Data Memory Unit*


Similar to Instruction Memory Unit, only that it can be written into as well

Two input ports for address and data, one output port (for data read out)


Two control signals: for Read and Write operations

b: *Sign Extension Unit*


Extends 16-bit input operand to 32 bits

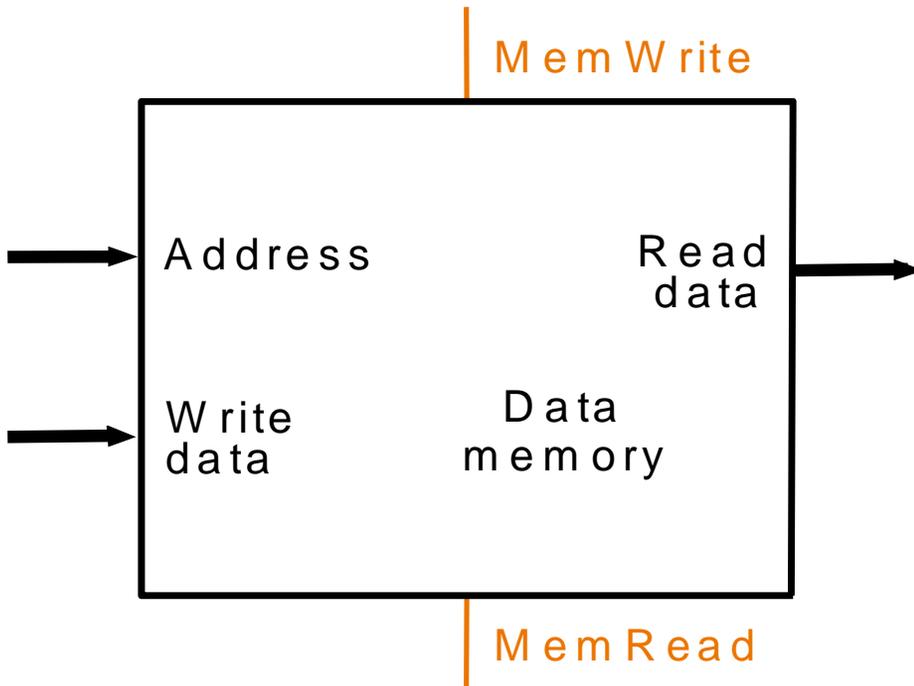

a. Data memory unit


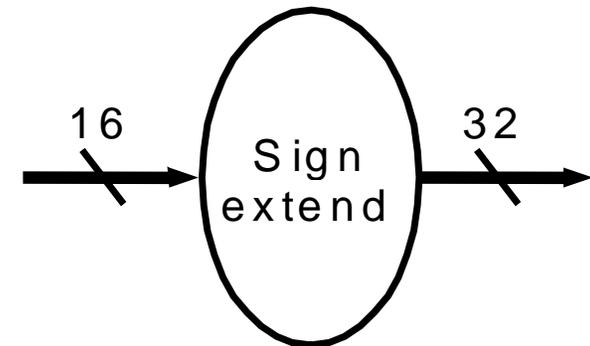


b. Sign-extension unit

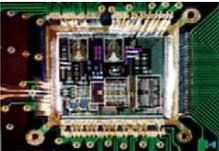



Datapath for Instruction Fetch (Piece I)

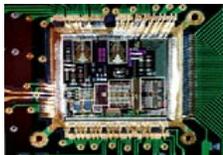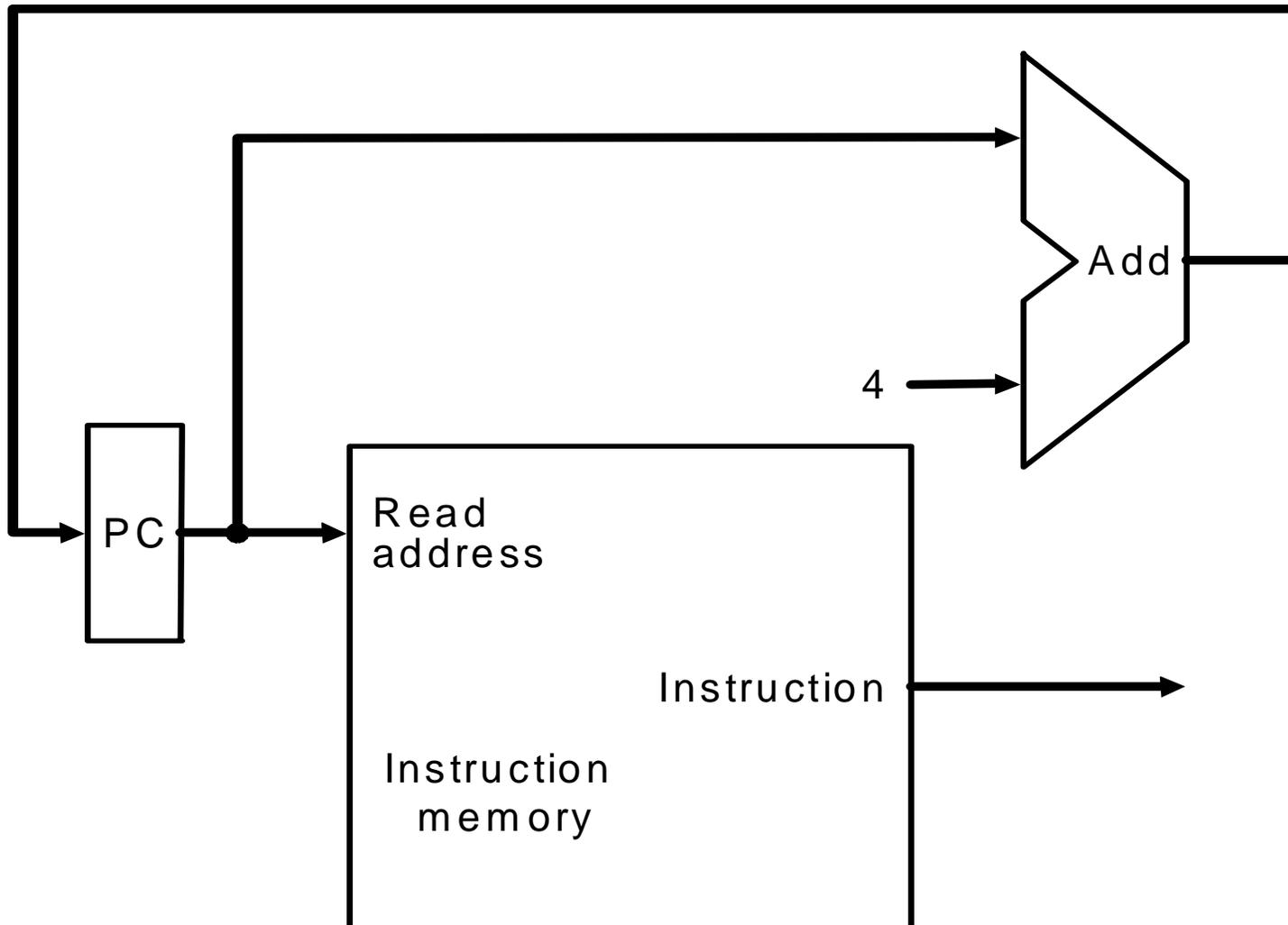- Fetching Instructions and Incrementing the program counter by 4





Datapath for R-type Instructions (Piece II)

- Datapath for R-type Instructions

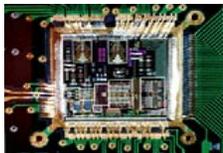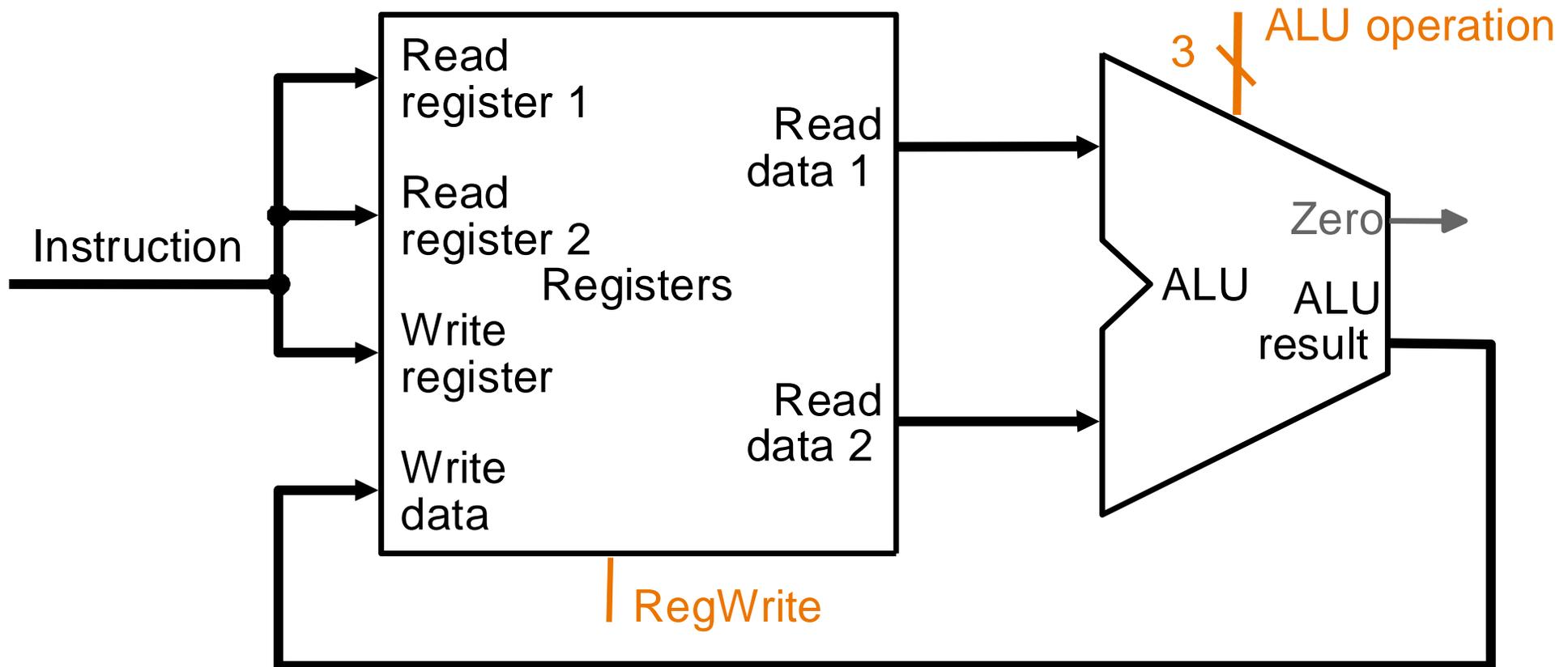



Datapath for Load/Store (Piece III)

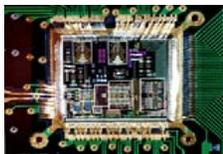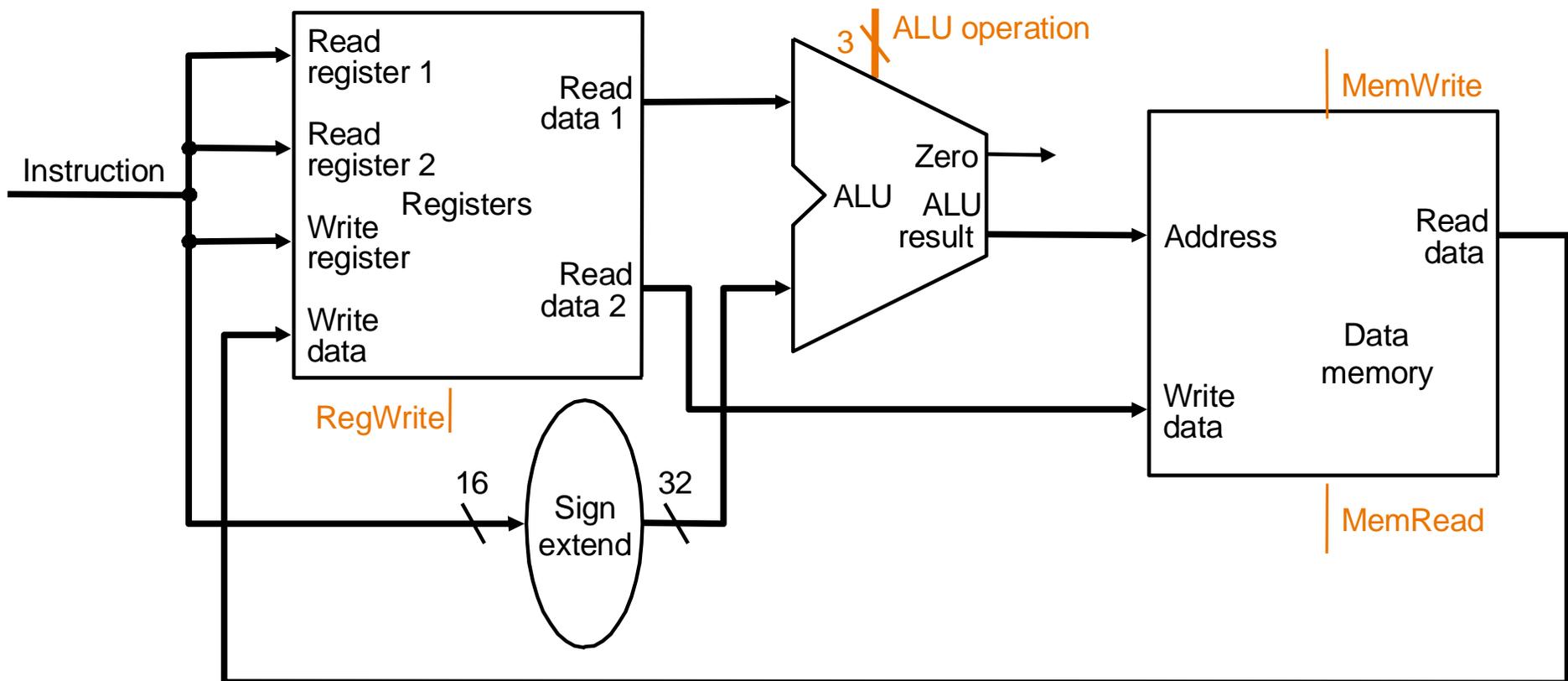- Datapath for load or store
 - (1) Register Access; (2) Memory Address calculation; (3) Read/Write
 - (4) Write into Register file (if the instruction is a *load*)




Datapath for Branch (Piece IV)

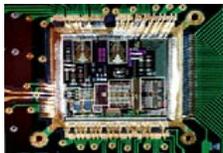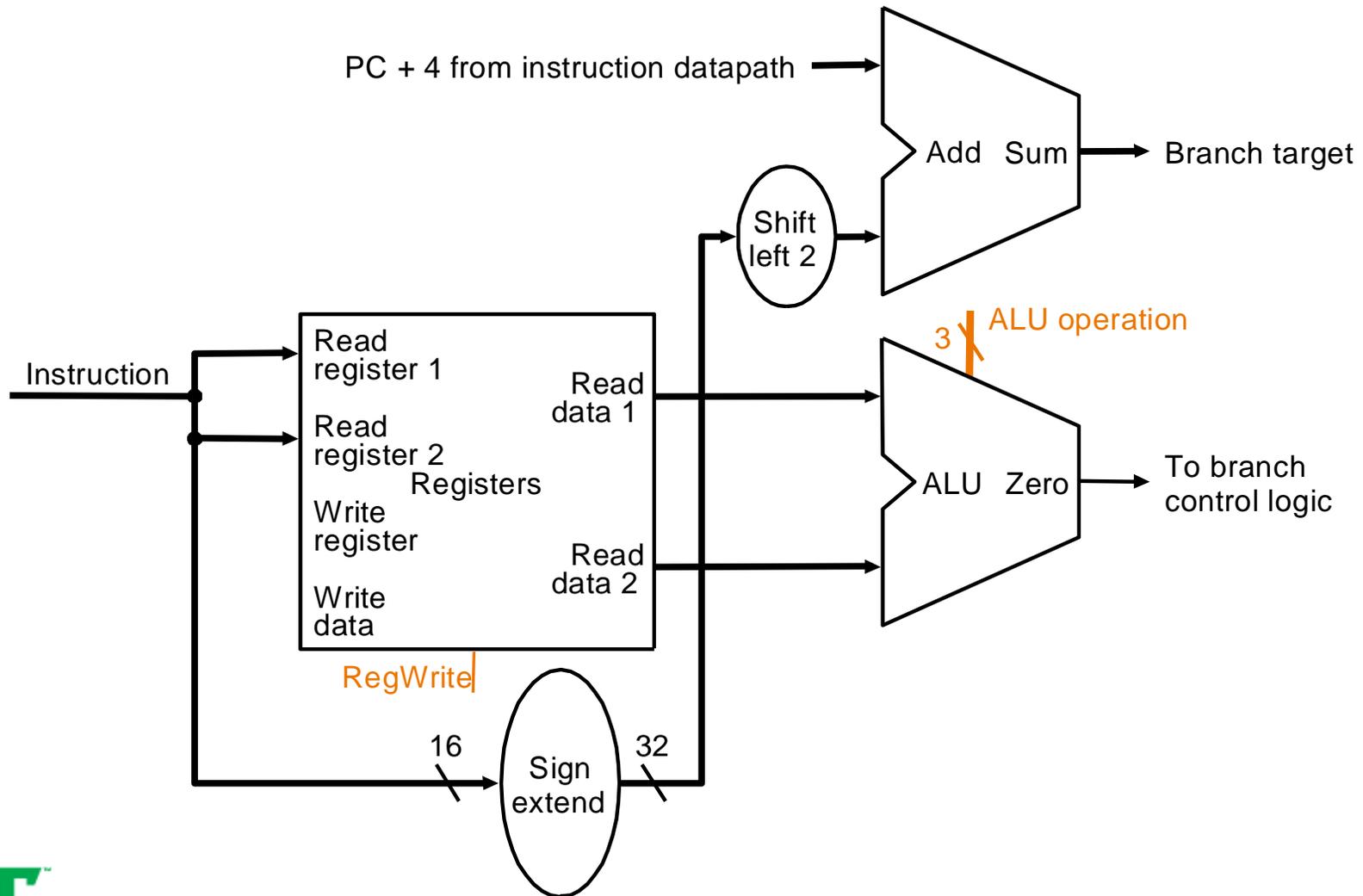- Unit “Shift left 2” adds “00” at the low-order end of the sign-extended offset
- Control logic is used to decide whether the incremented PC or branch target should replace the PC based on the “Zero” output of the ALU




Datapath Construction Strategy

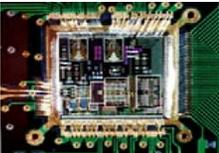- Now, we have “pieces” of datapath that are capable of performing distinct functions
- We want to “stitch” them together to yield a final datapath that can execute all the instructions (lw, sw, add, sub, and, or, slt, beq, j)
- We will use multiplexors (or muxes for short) for stitching the datapath





Datapath Construction (Merge Pieces II & III)

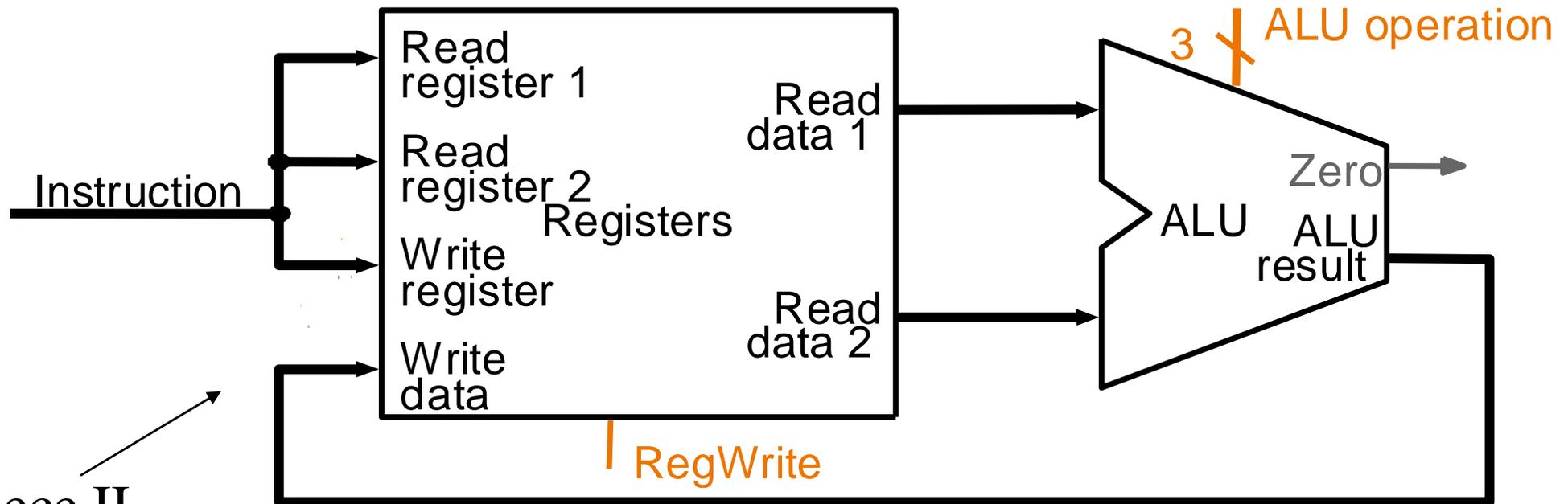

Piece II



+

Piece III

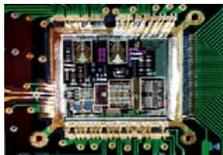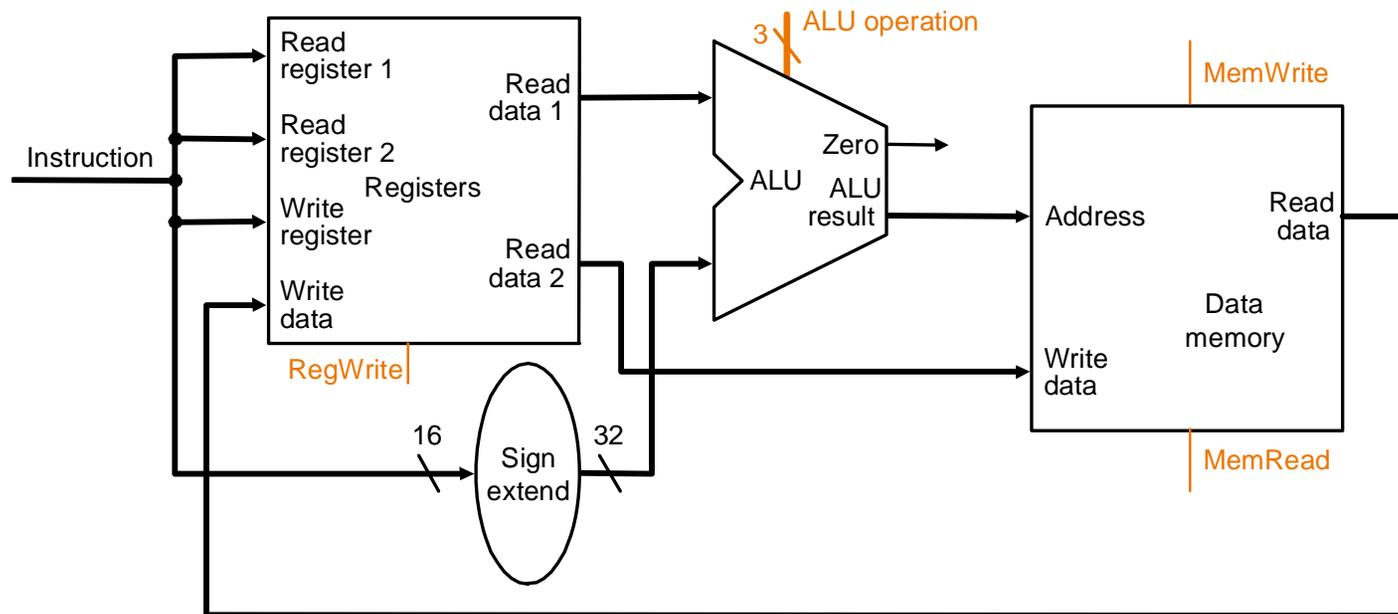



And you will get..

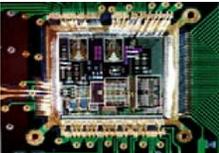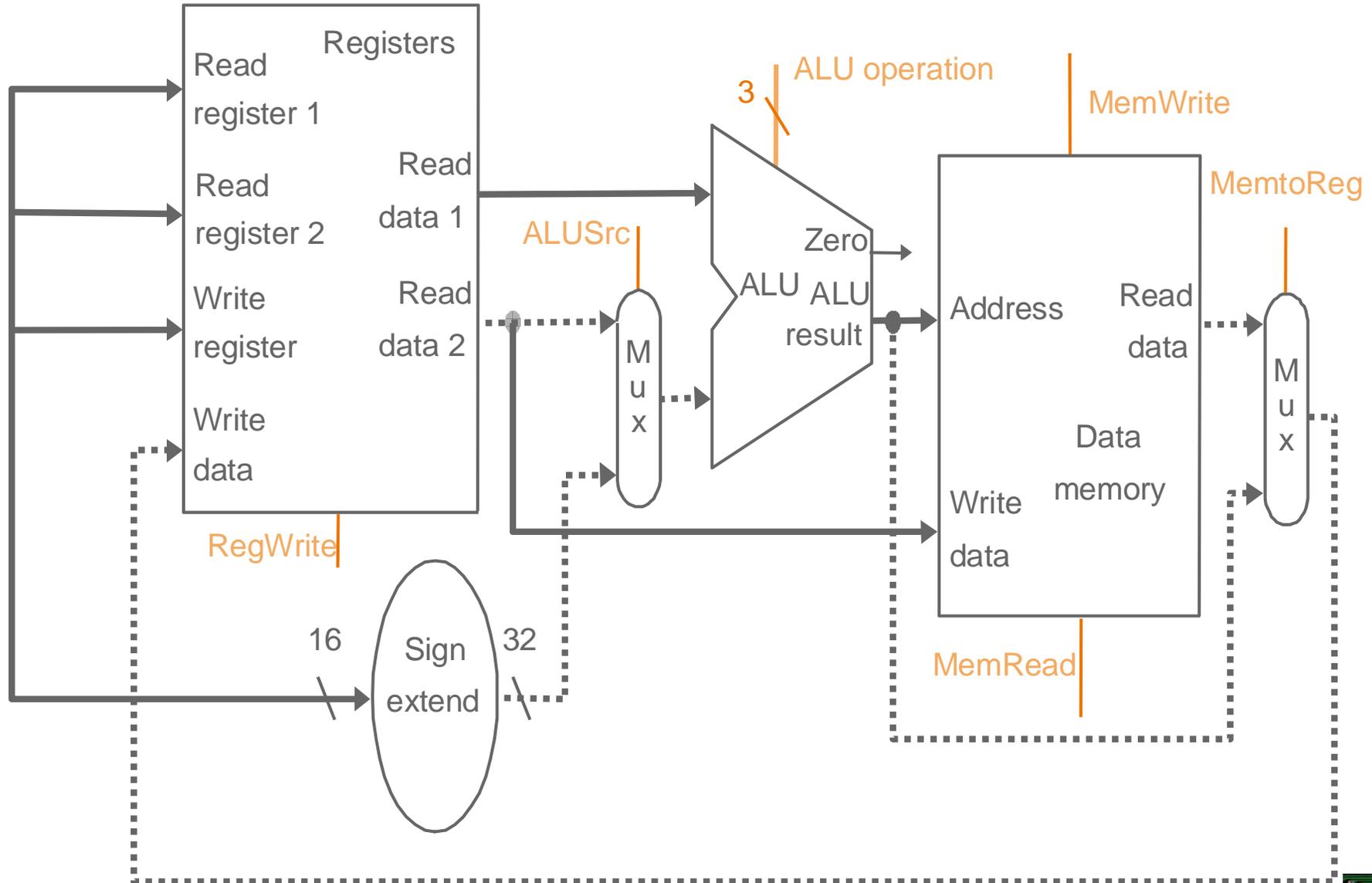- **Rule: Whenever we have more than one input feeding a functional unit, introduce a multiplexor (this gives rise to a control signal, more later..)**





Datapath Construction ... *contd* (merge Piece I)

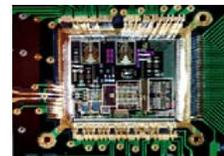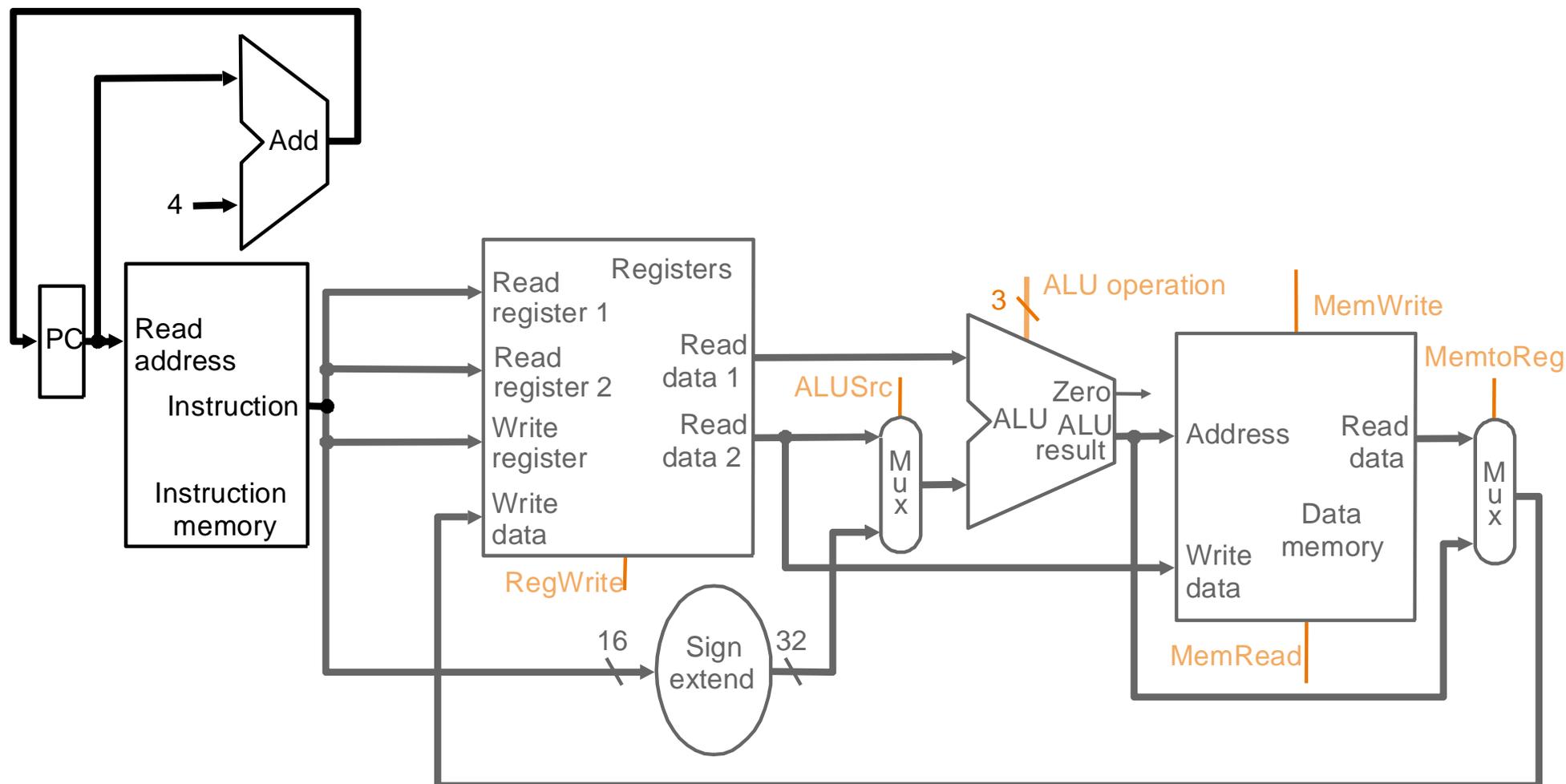
- Just tack the Instruction Fetch and PC increment logic at the front!



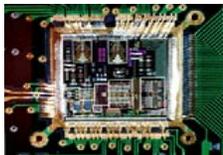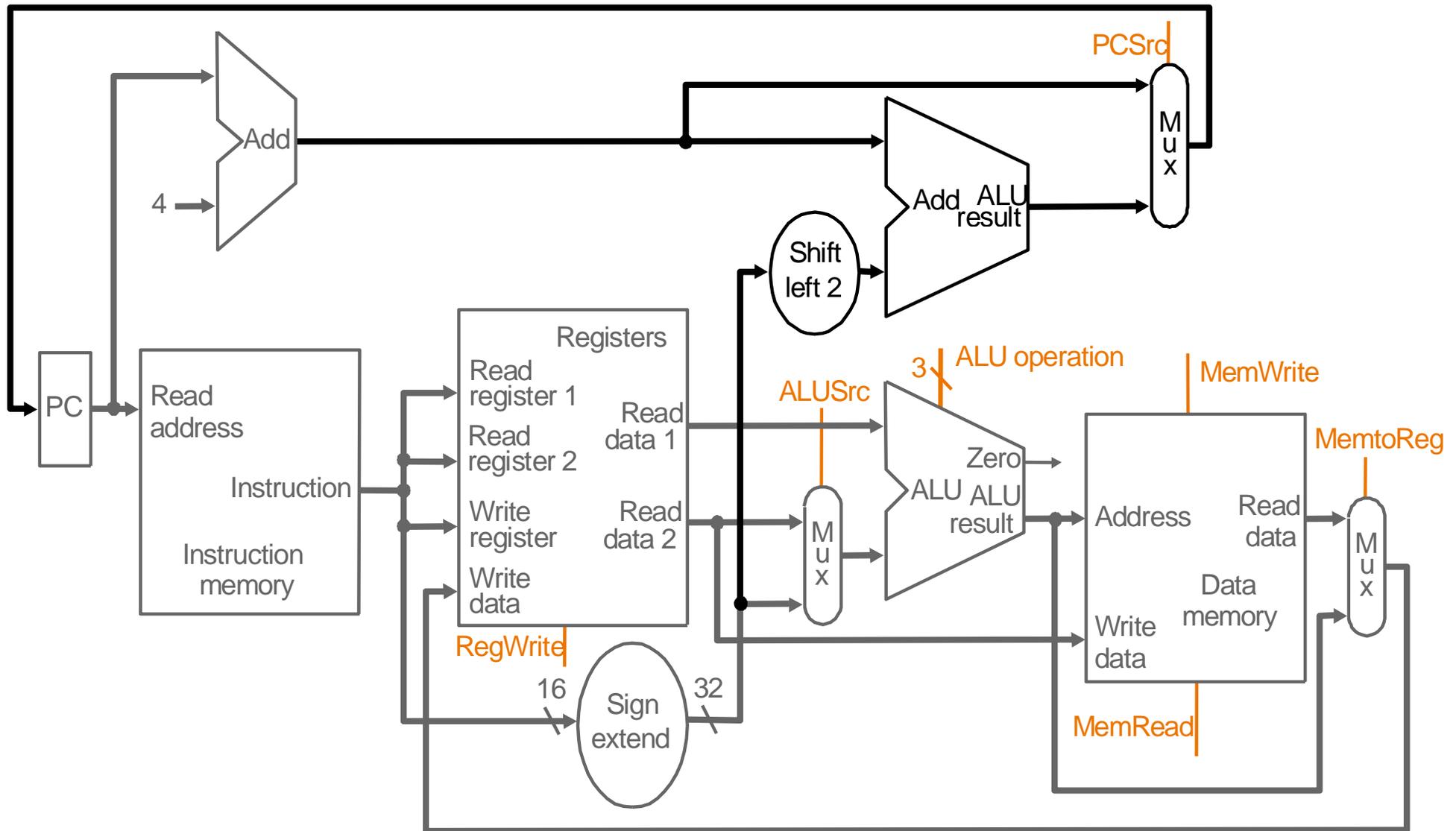
Datapath Construction (Finally, merge Piece IV)



Final Datapath

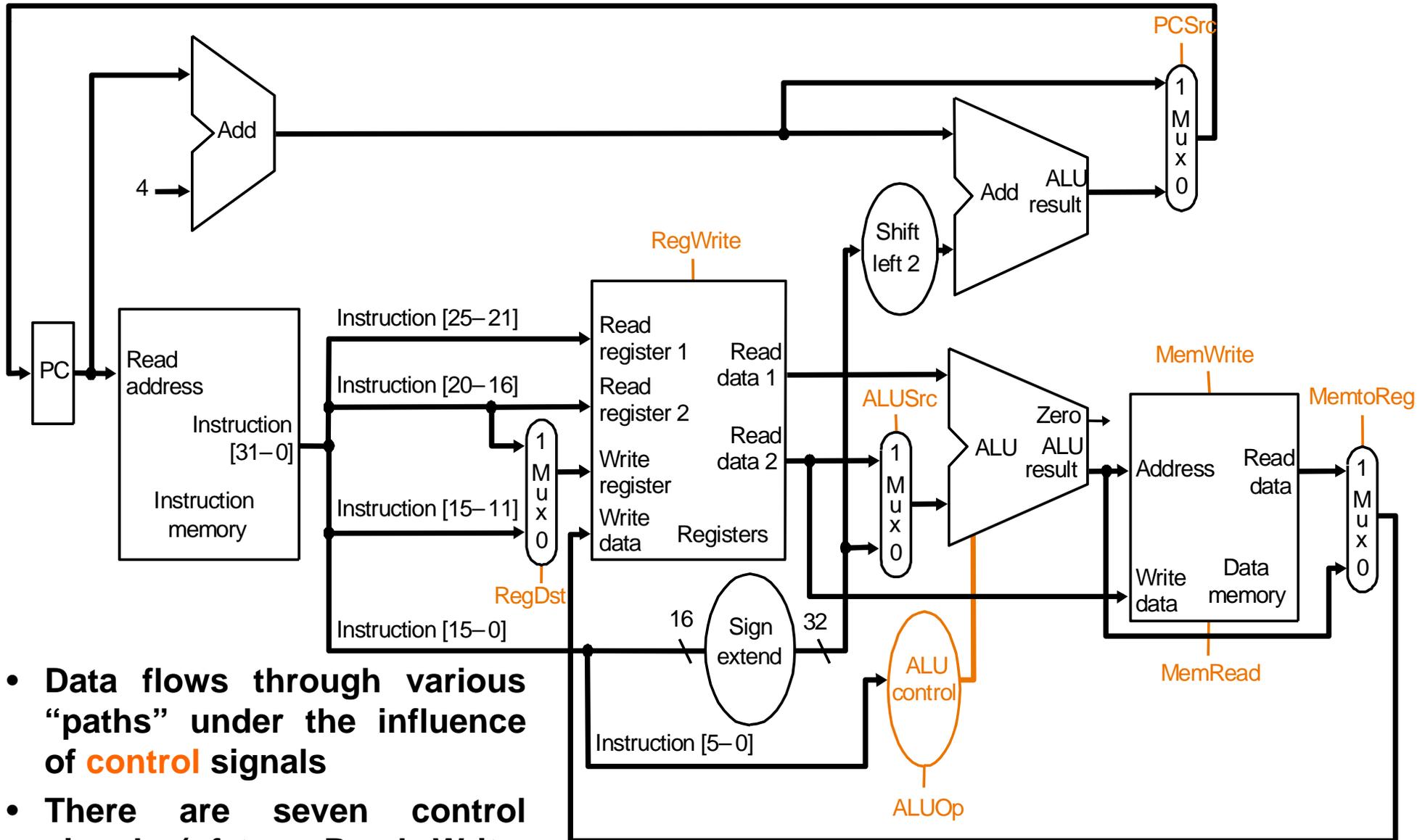

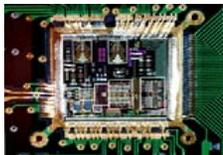- Data flows through various “paths” under the influence of **control** signals
- There are seven control signals (of type Read, Write, or Mux Select)




Defining the Control..

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction
- Example:

add \$8, \$17, \$18 Instruction Format:

000000	10001	10010	01000	00000	100000
op	rs	rt	rd	shamt	funct


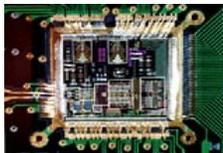
- ALU's operation based on instruction type and function code
- We will design two control units:
 - (1) *ALU Control* to generate appropriate function select signals for the ALU
 - (2) *Main Control* to generate signals for functional units other than the ALU




ALU Control - Truth Table & Implementation

Describe it using a truth table (can turn into gates):

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

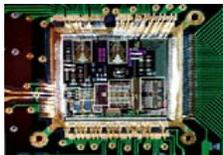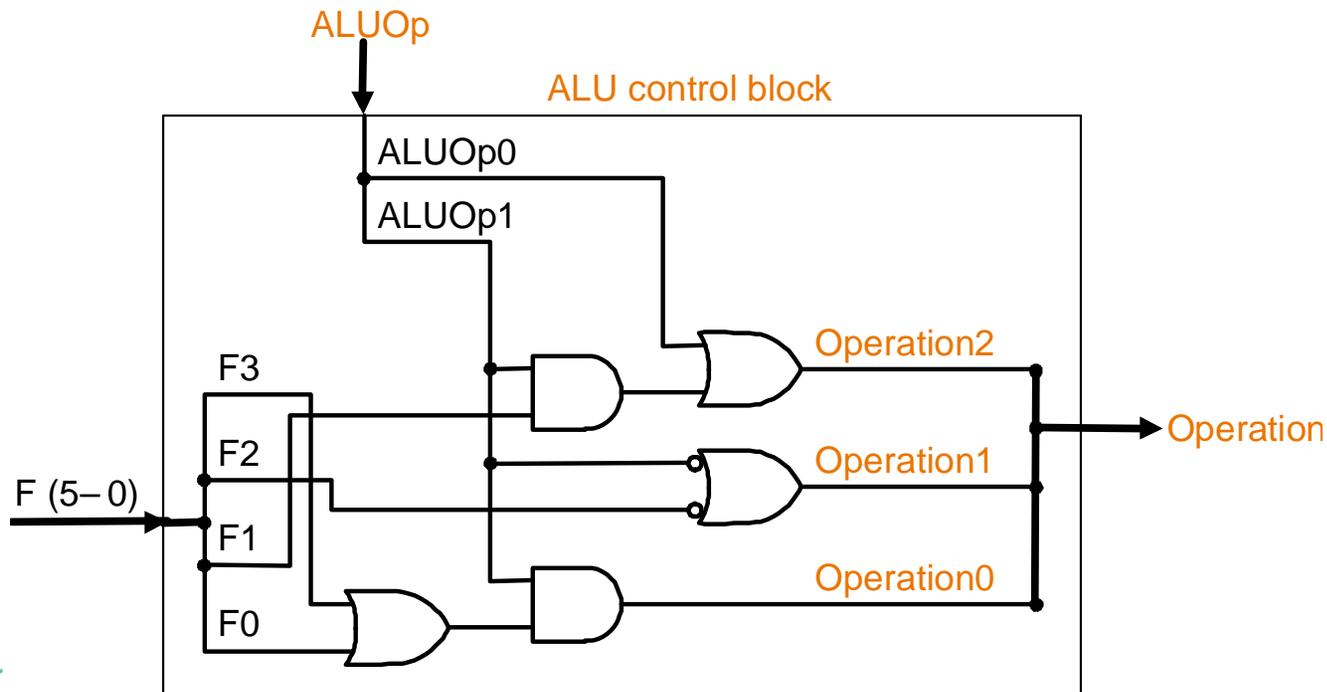


Designing the Main Control

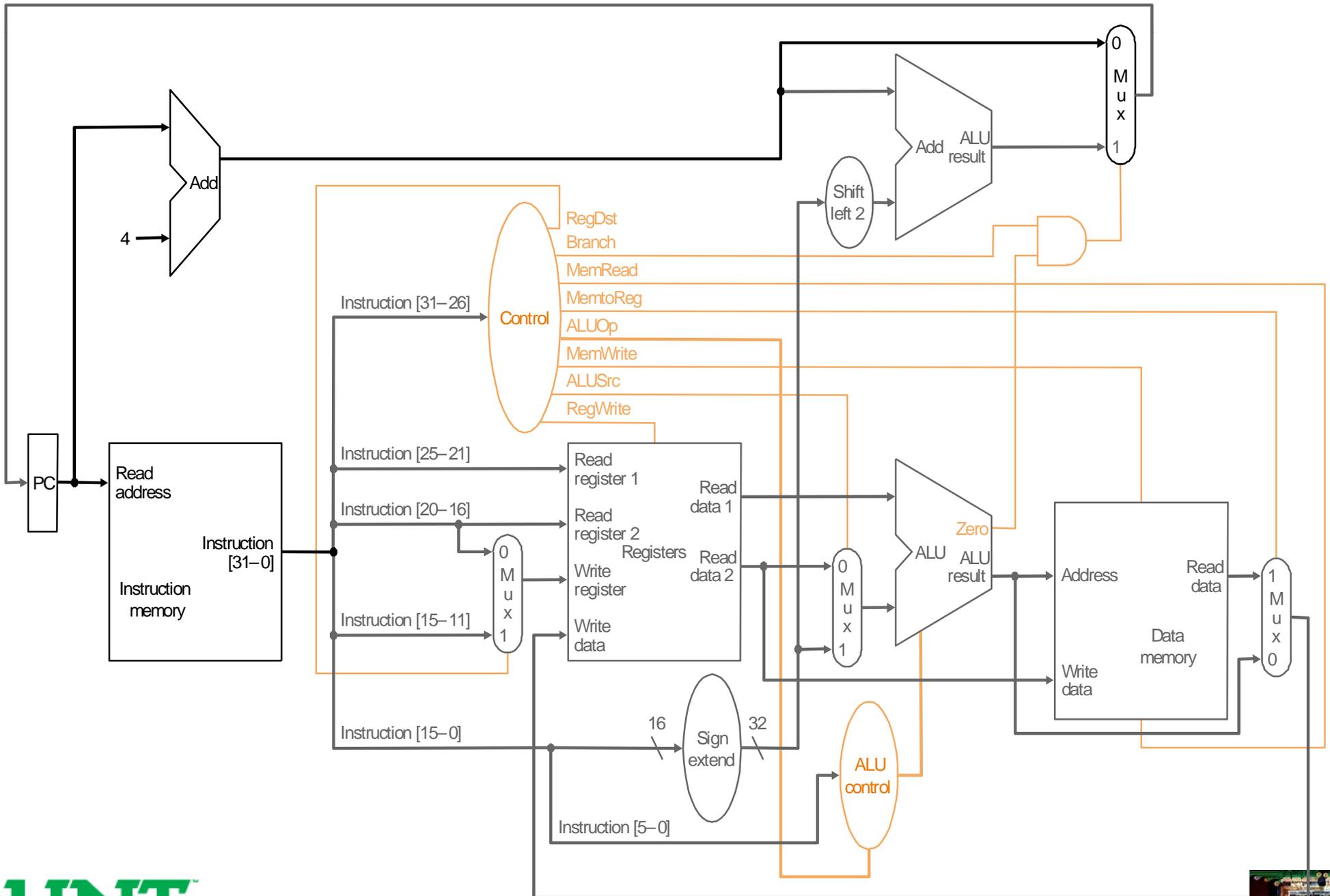

Control Signals and their Effects



Signal Name	Effect When deasserted	Effect when asserted
RegDst	The register destination number for the Write register comes from the rt field (bits 20-16)	The register destination number for the Write register comes from the rd field (bits 15-11)
RegWrite	NONE	The register on the Write register input is written with the value on the Write data input
ALUSrc	The second ALU operand comes from the second register file output (Read data 2)	The second ALU operand is the sign-extended lower 16 bits of the instruction
PCSrc	The PC is replaced by the output of the adder that computes the value of PC + 4.	The PC is replaced by the output of the adder that computes the branch target
MemRead	None	Data Memory contents designated by the address input are put on the Read data output
MemWrite	None	Data memory contents designated by the address input are replaced by the value on the Write data input
MemtoReg	The value fed to the register Write data input comes from the ALU	The value fed to the register Write data input comes from the data memory.

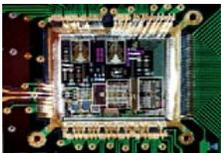

Main Control: Truth Table & Implementation


Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Inputs

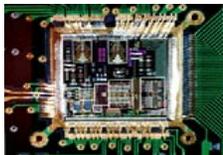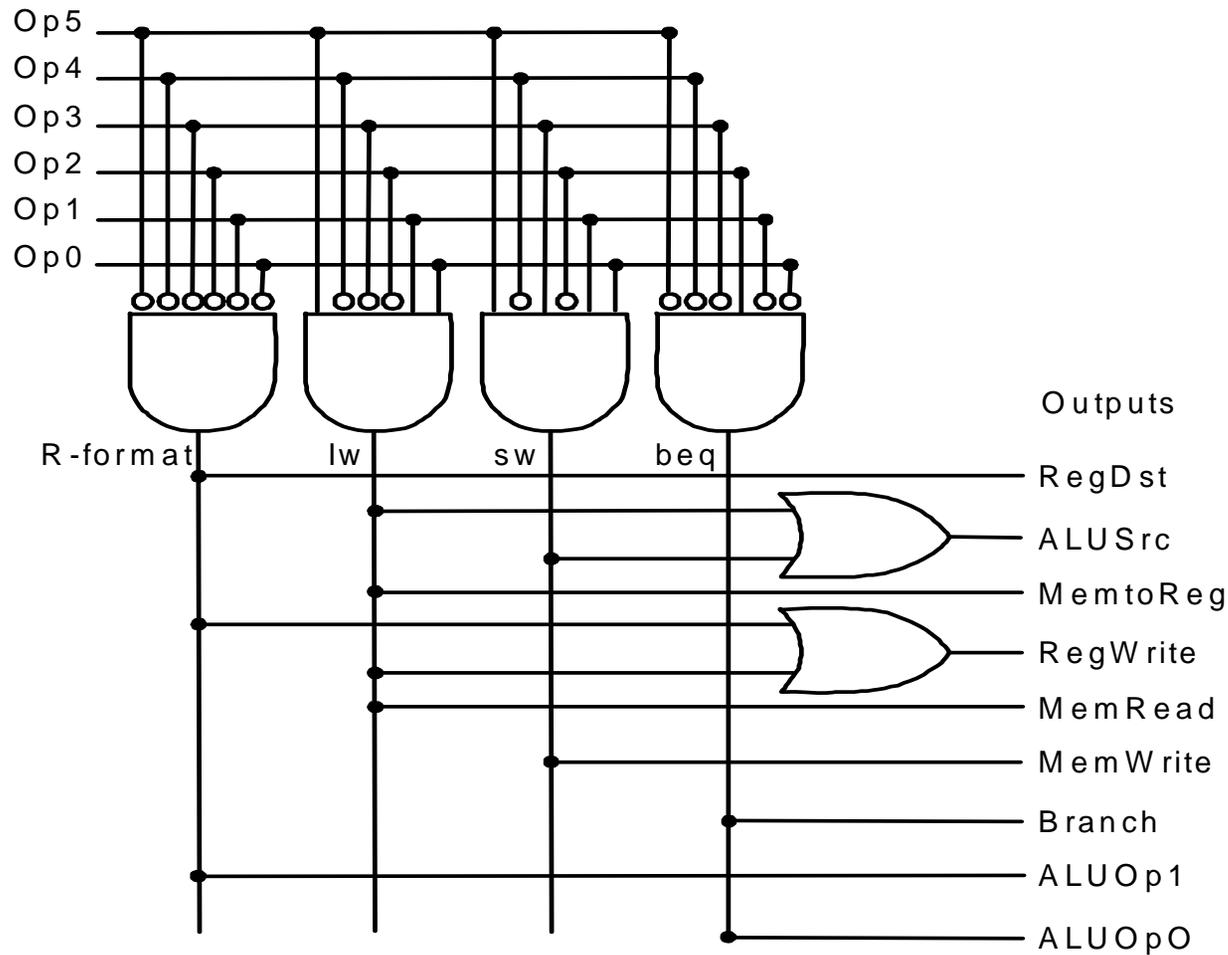


Our Simple Control Structure

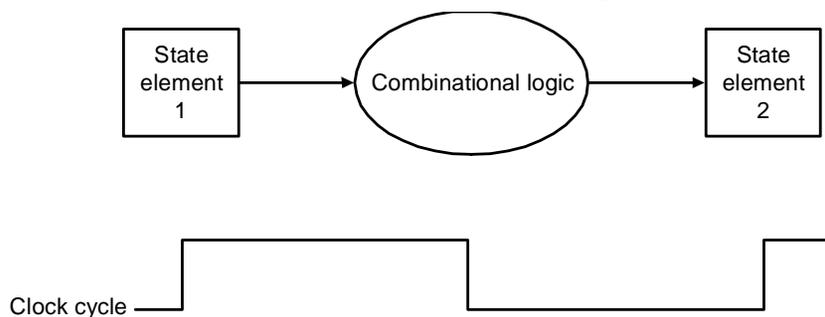- All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
 - ALU might not produce “right answer” right away
 - we use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path



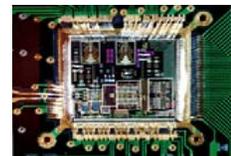We are ignoring some details like setup and hold times





How does the single cycle datapath works?



- Let us understand this by highlighting the portions of the datapath when an R-type instruction is executed
- For an R-type instruction we go through the following phases:
 - Phase 1: Instruction Fetch
 - Phase 2: Register File Read
 - Phase 3: ALU execution
 - Phase 4: Write the Result into the Register File
- **NOTE:** All the four phases are completed in only ONE clock cycle and hence it is a “single cycle implementation”



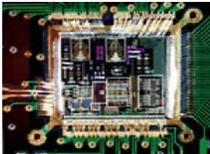
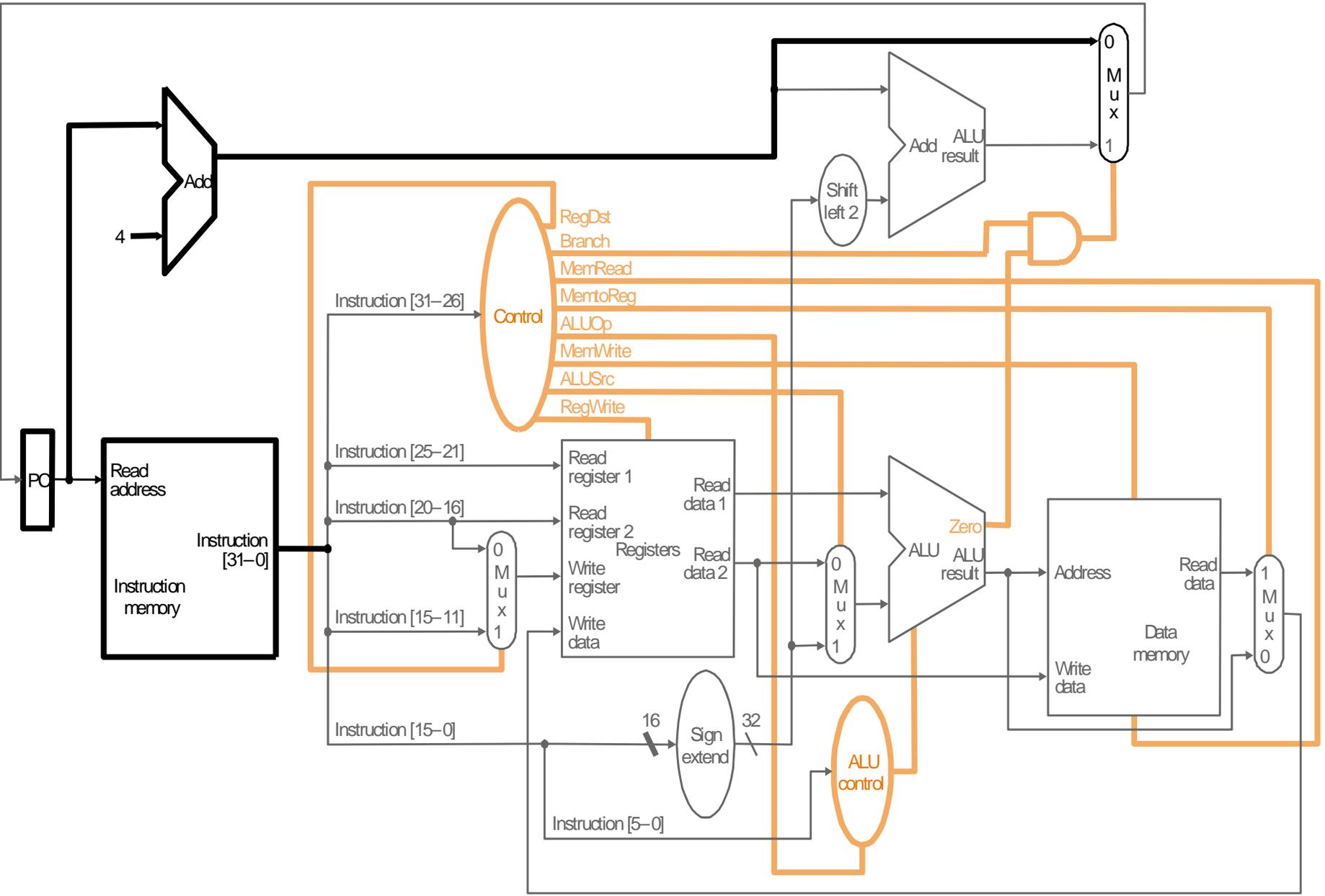
R-type Instruction – Phase 1 (Instruction Fetch)



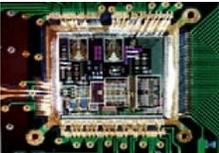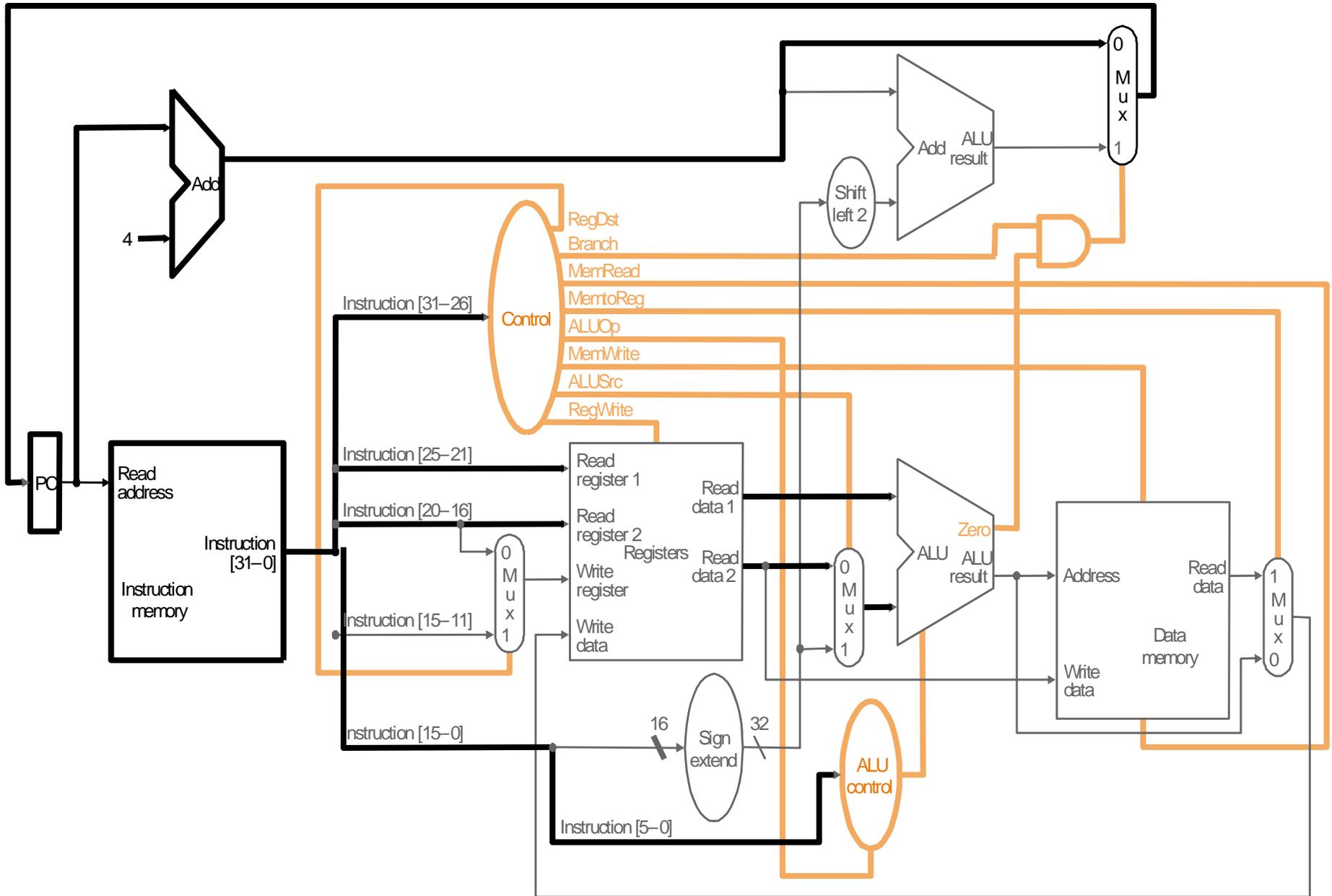
R-type Instruction – Phase 2 (Register Read)



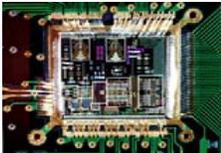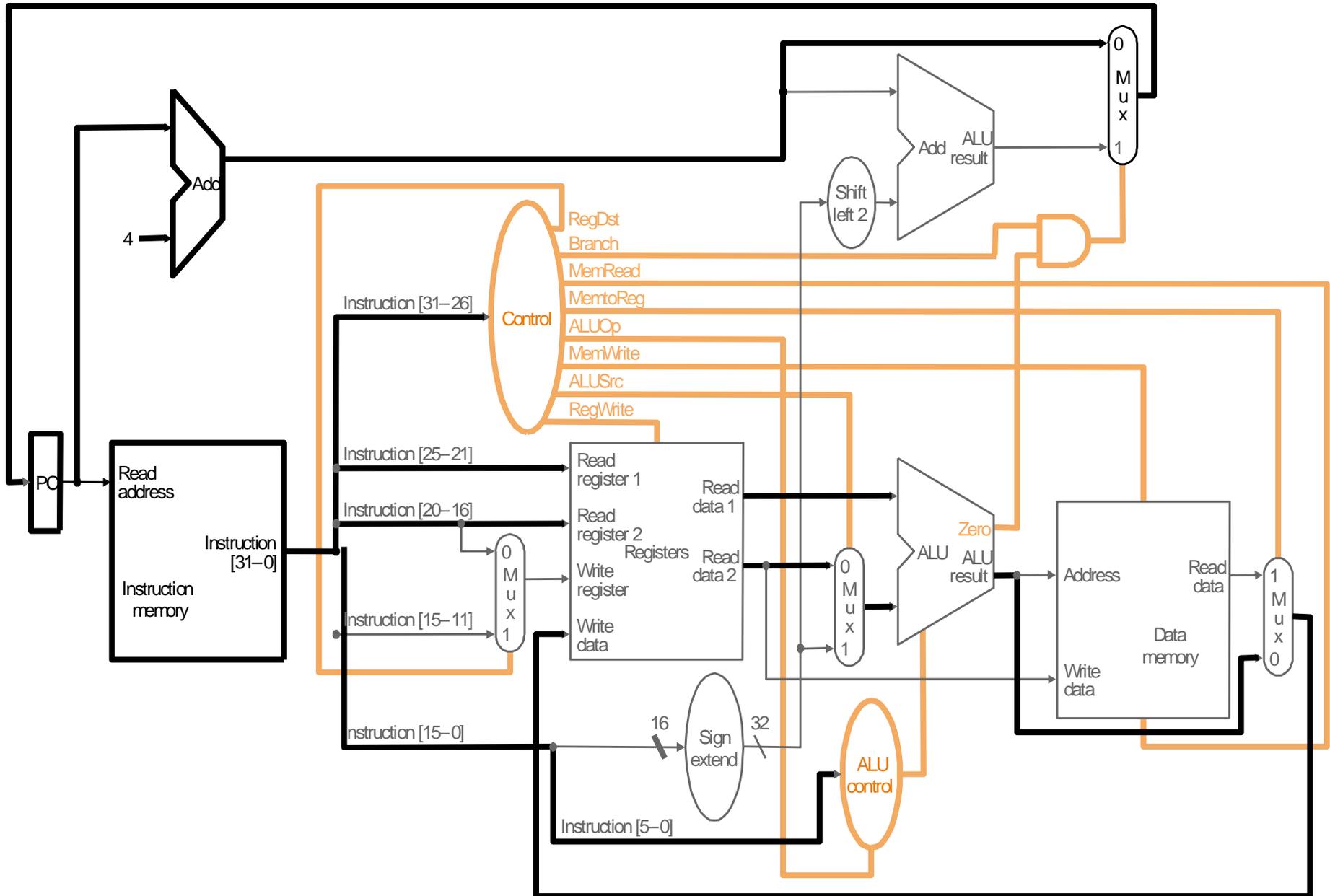R-type Instruction – Phase 4 (Write the Result)



How do we handle jump?

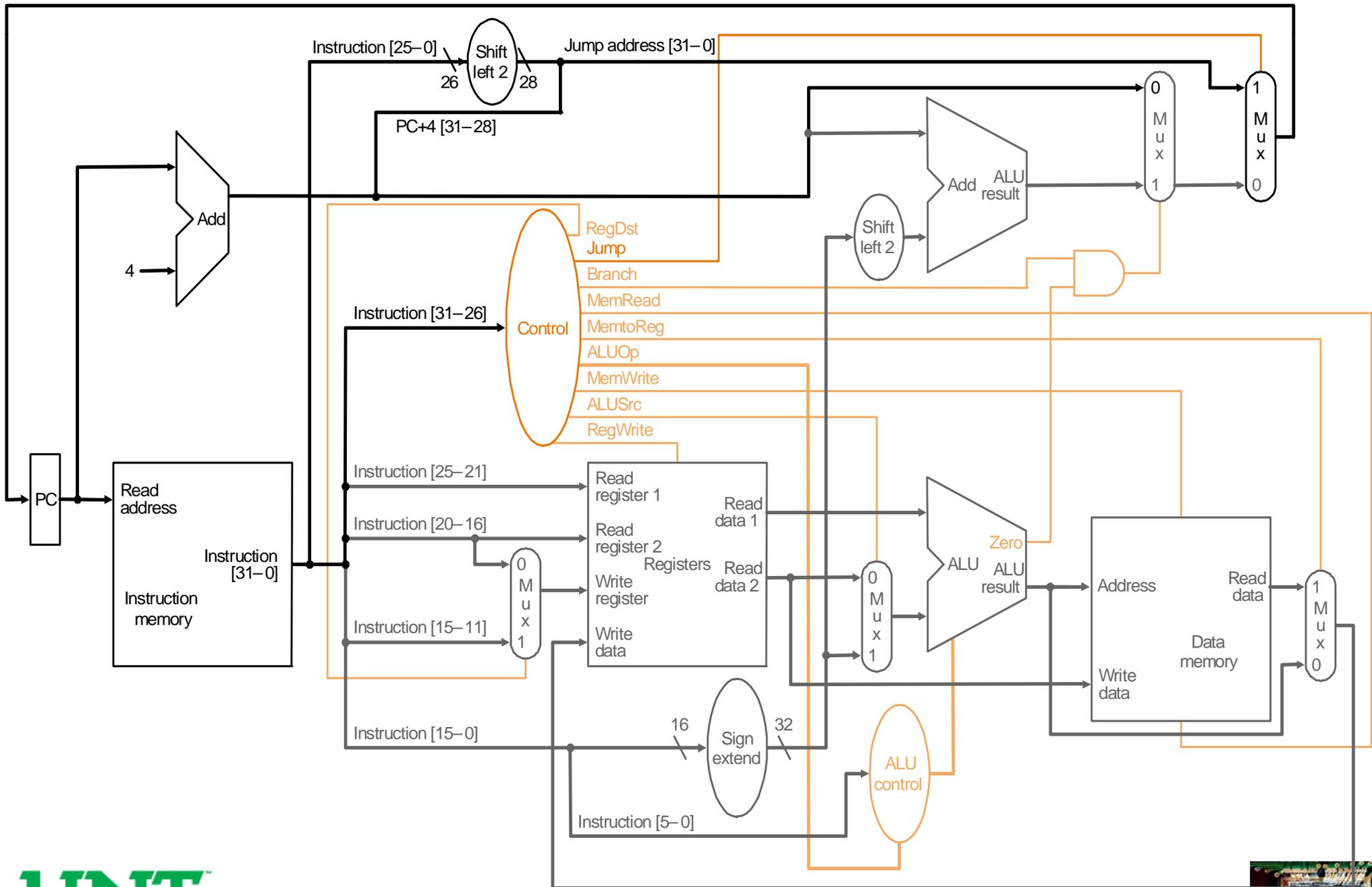


Where we are headed

- Single Cycle Problems:
 - what if we had a more complicated instruction like floating point?
 - wasteful of area
- One Solution:
 - use a “smaller” cycle time
 - have different instructions take different numbers of cycles
 - a “multicycle” datapath:




Single Cycle Implementation: Summary

- All instructions are executed in only clock cycle
- We built a single cycle datapath from scratch
- We designed appropriate controller to generate correct correct signals
- All instructions are not born equal; that some require more work, some less => disadvantage of single cycle implementation is that the slowest instruction determines the clock cycle width
- In reality, no body implements single cycle approach
- Suggestion: STARE, STARE, STARE at the single cycle datapath to familiarize yourself
- Given the single cycle datapath, you should be able to “highlight” active portions of the datapath for any given instruction (just as we did for an R-type instruction in the class)

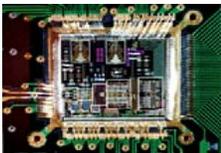


Single Cycle Implementation - Recap


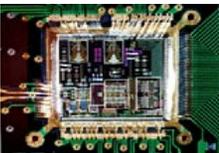
- Single Cycle Problems:
 - what if we had a more complicated instruction like floating point?
 - wasteful of area
 - Cycle width determined by the slowest instruction
- One Solution:
 - use a “smaller” cycle time
 - have different instructions take different numbers of cycles
 - a “multicycle” datapath:





Multicycle Approach – High Level View

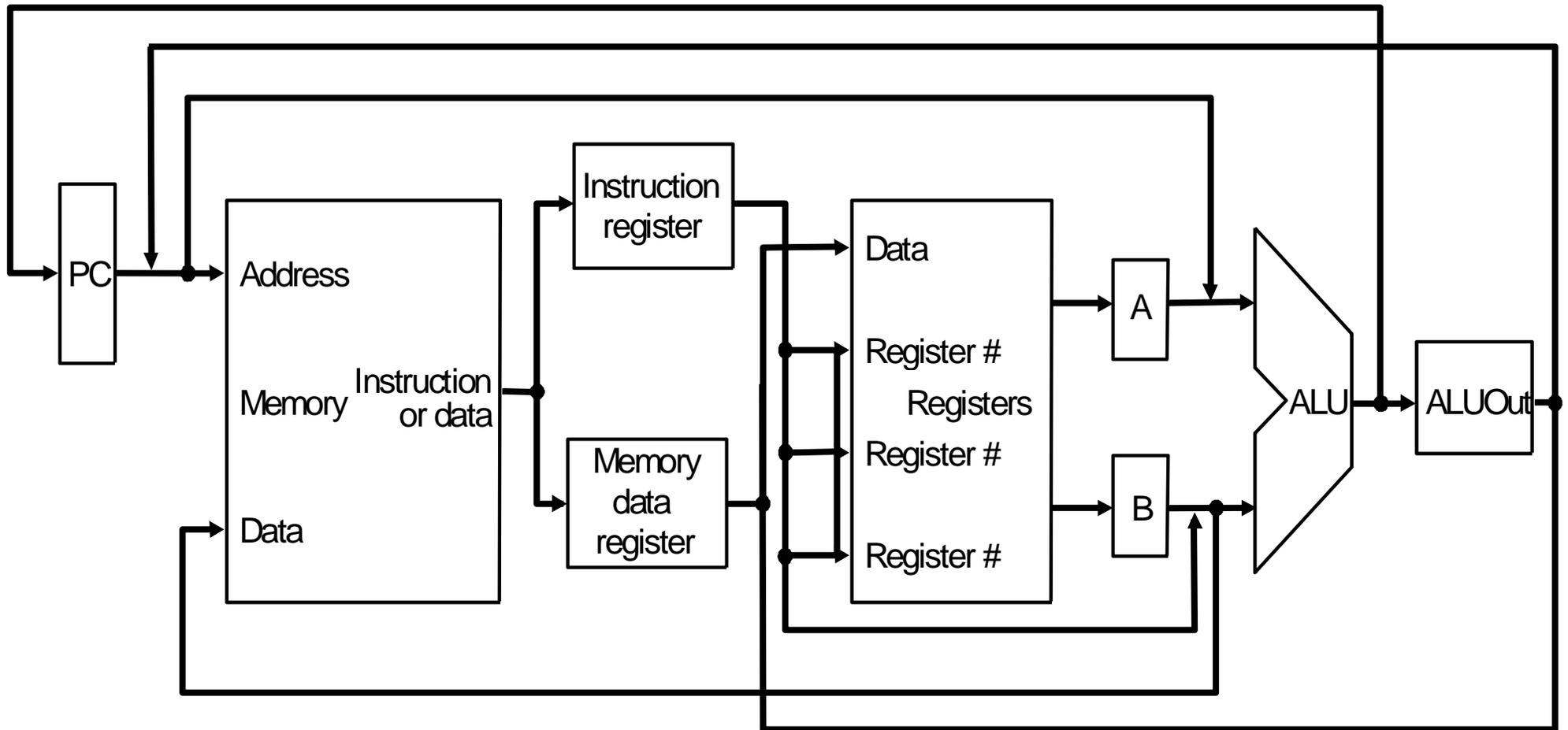

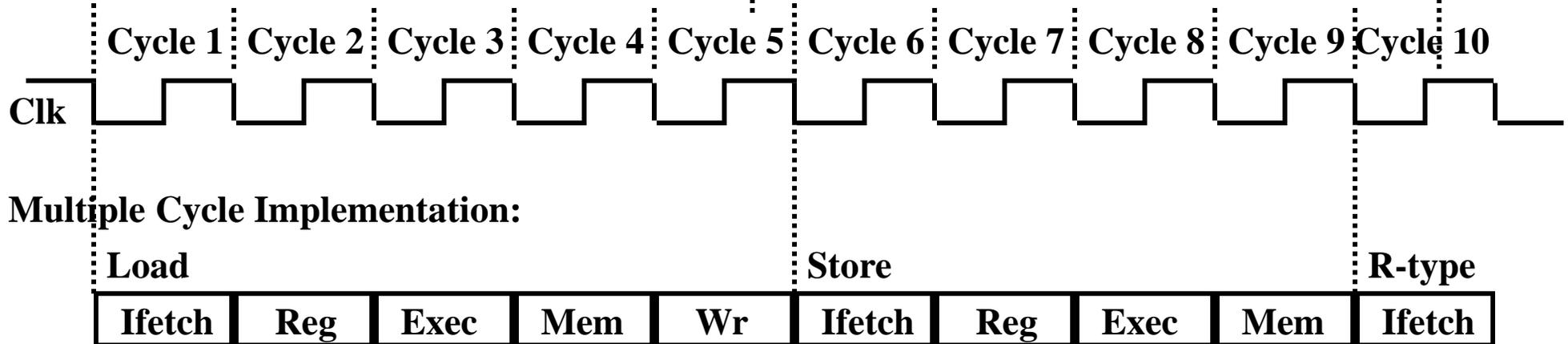
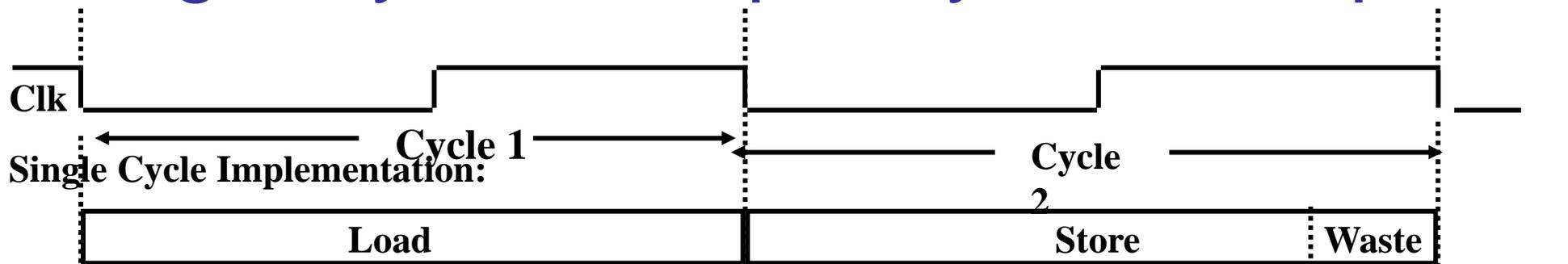
Single Cycle, Multiple Cycle, vs. Pipeline




Pipeline Implementation:

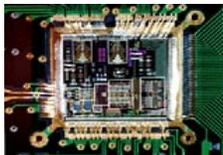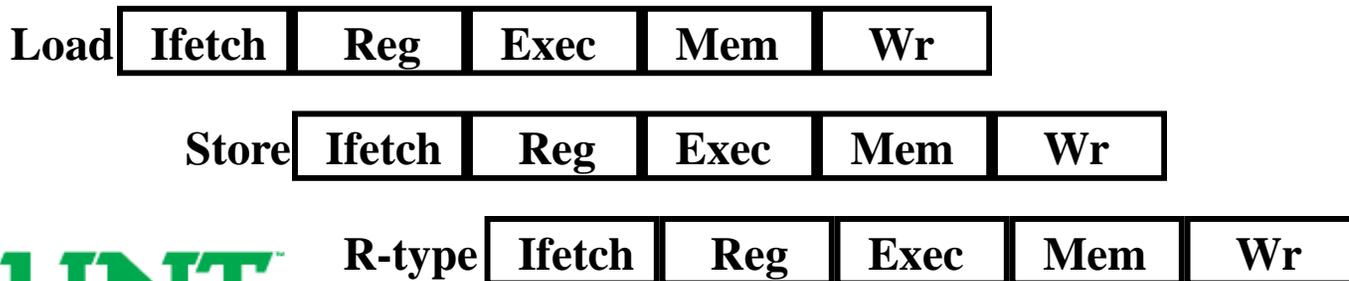



Basic Idea

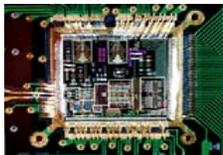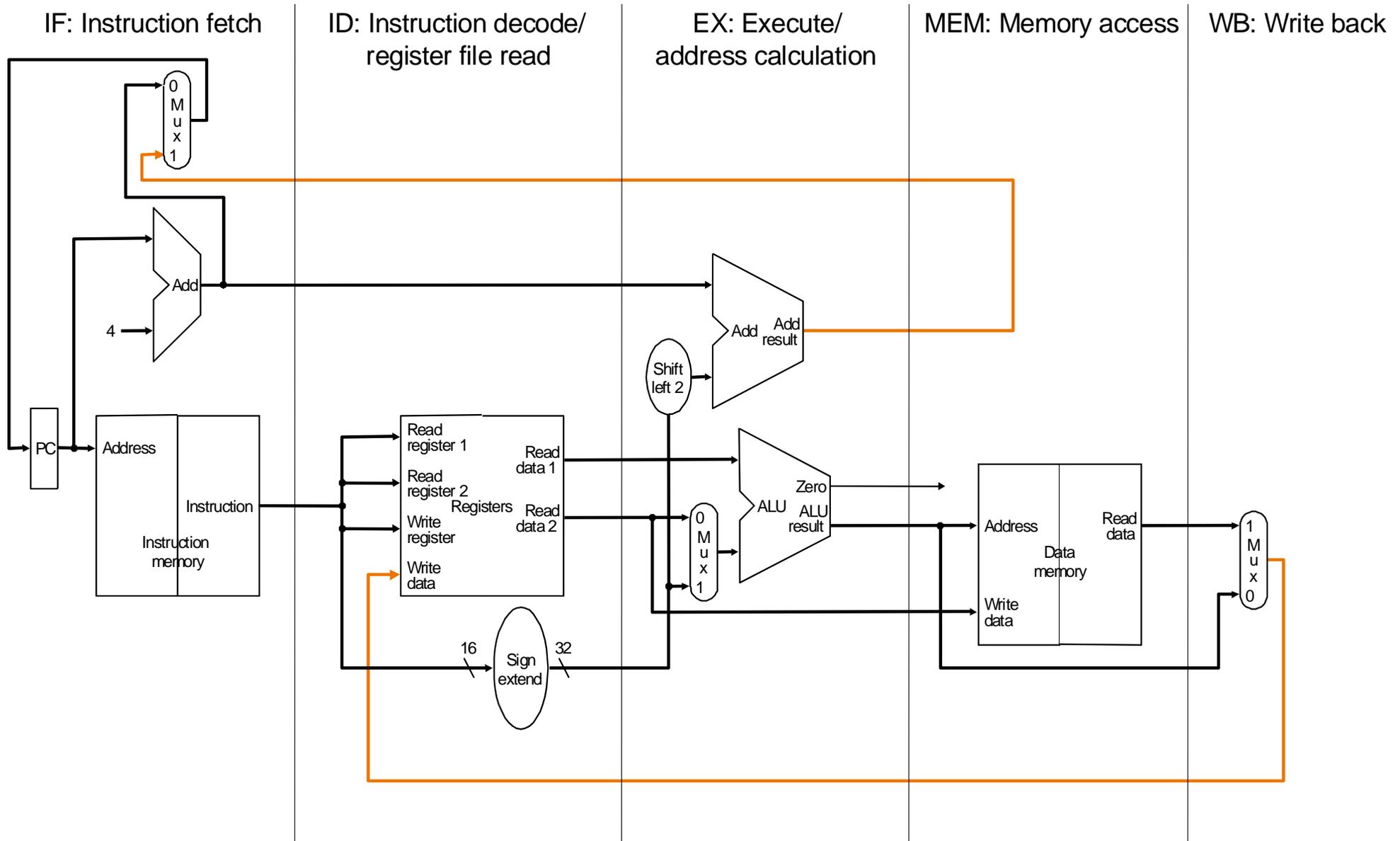

Corrected Datapath

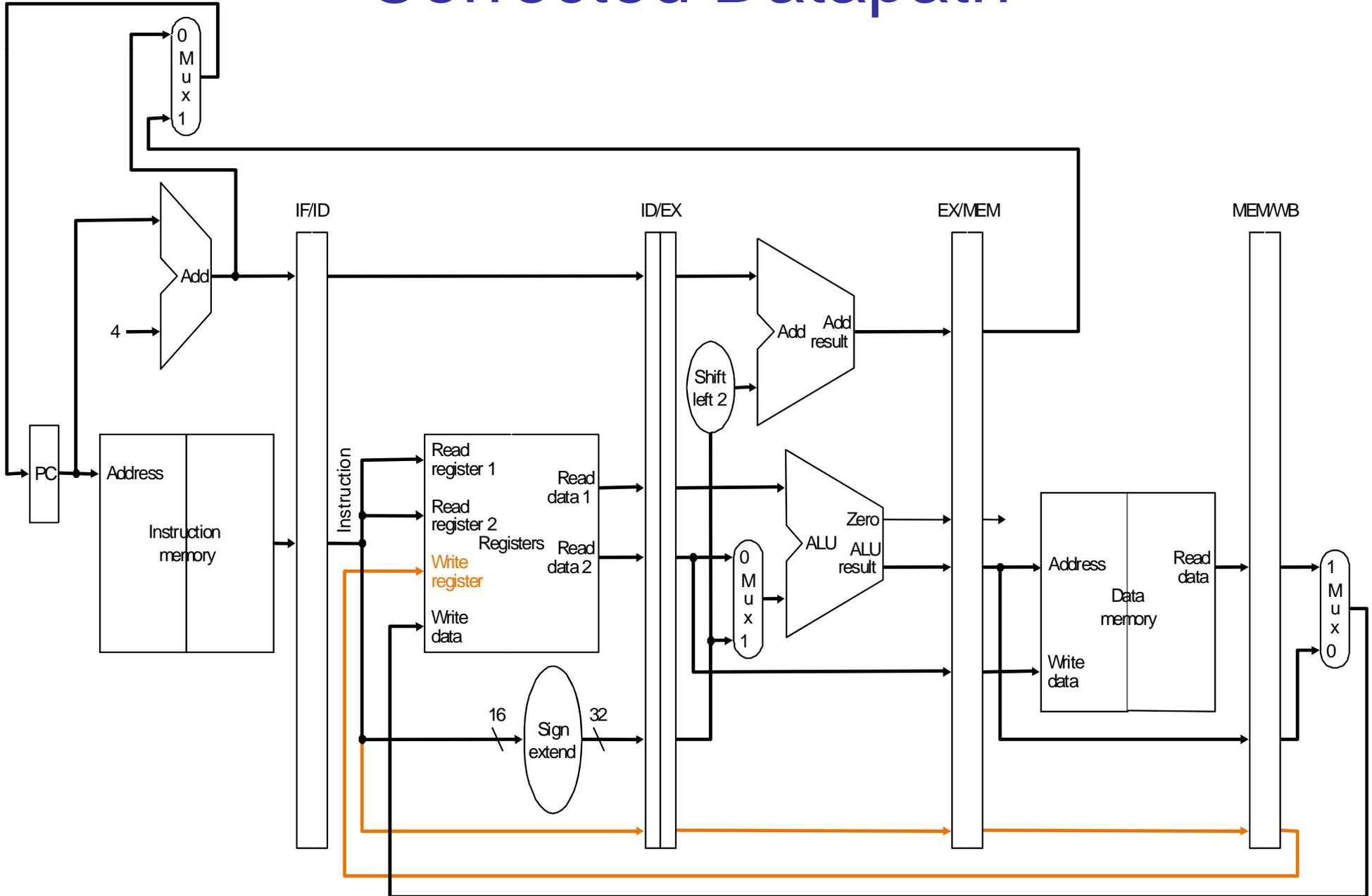

Datapath with Control

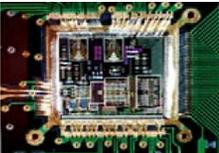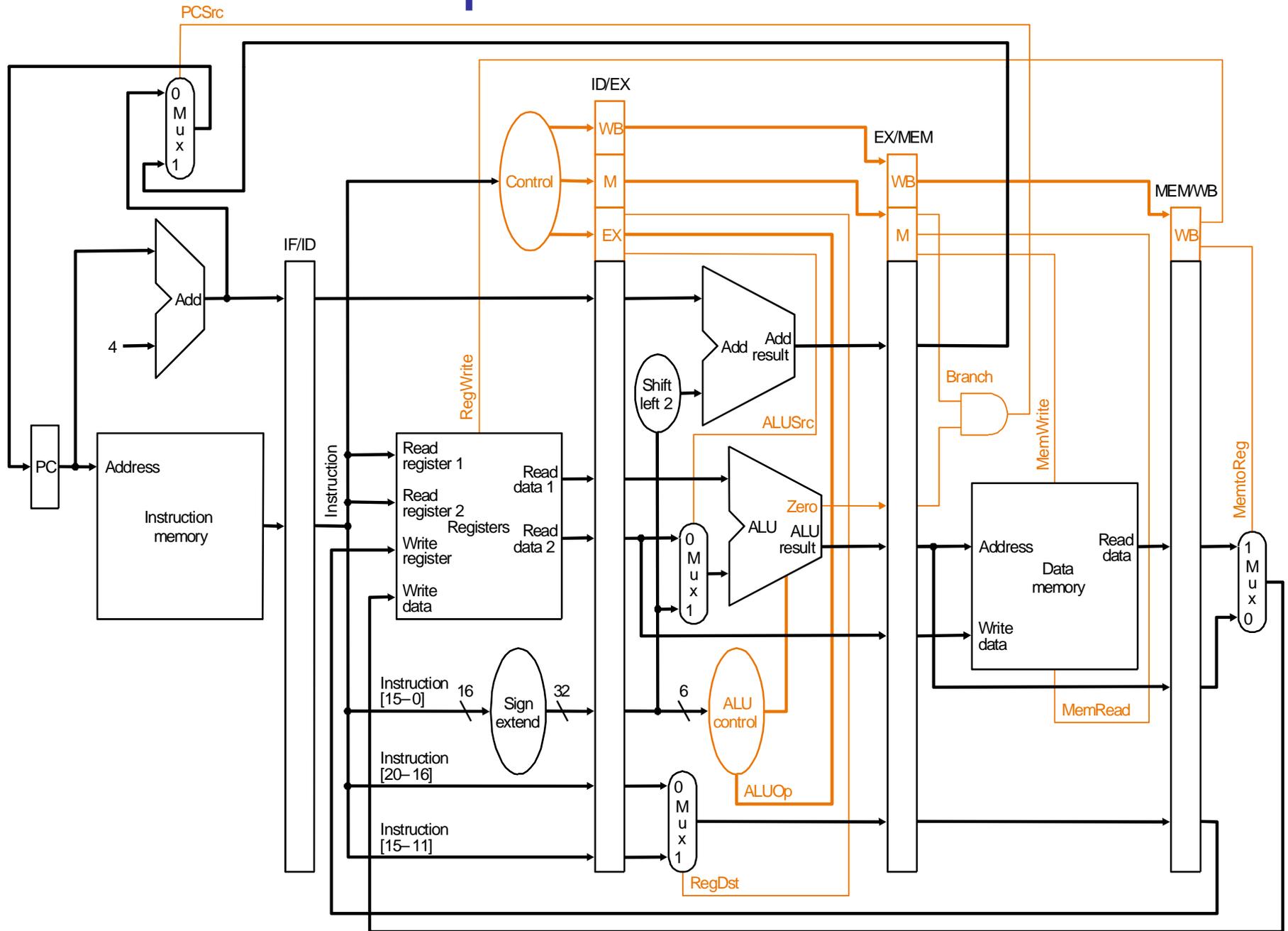

Pipelining Summary

- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- **Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number pipe stages**
- Pipeline rate limited by **slowest** pipeline stage
- Unbalanced lengths of pipe stages reduces speedup
- Time to “**fill**” pipeline and time to “**drain**” it reduces speedup
- Three types of pipeline hazards: structural, data, and control/branch
- Stalling helps any kind of hazard
- Data hazard solutions: Stalling, Data forwarding, Hazard detection
- Control or Branch Hazard solutions: Stalling, Branch Prediction, Delayed Branching

